

Question 1(a) [3 marks]

Explain De-Morgan's theorem for Boolean algebra

Answer:

De-Morgan's theorem consists of two laws that show the relationship between AND, OR, and NOT operations:

Law 1: The complement of a sum equals the product of complements

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

Law 2: The complement of a product equals the sum of complements

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

Table: De-Morgan's Laws Verification

A	B	A+B	$\overline{A + B}$	\overline{A}	\overline{B}	$\overline{A} \cdot \overline{B}$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

Mnemonic: "NOT over OR becomes AND of NOTs, NOT over AND becomes OR of NOTs"

Question 1(b) [4 marks]

Convert following decimal number into binary and octal number (i) 215 (ii) 59

Answer:

Binary Conversion:

For 215:

- Divide by 2 repeatedly: $215/2 = 107$ remainder 1
- $107/2 = 53$ remainder 1
- $53/2 = 26$ remainder 1
- $26/2 = 13$ remainder 0
- $13/2 = 6$ remainder 1
- $6/2 = 3$ remainder 0
- $3/2 = 1$ remainder 1
- $1/2 = 0$ remainder 1
- Therefore, $(215)_{10} = (11010111)_2$

For 59:

- Divide by 2 repeatedly: $59/2 = 29$ remainder 1
- $29/2 = 14$ remainder 1
- $14/2 = 7$ remainder 0
- $7/2 = 3$ remainder 1
- $3/2 = 1$ remainder 1
- $1/2 = 0$ remainder 1
- Therefore, $(59)_{10} = (111011)_2$

Octal Conversion:**For 215:**

- Divide by 8 repeatedly: $215/8 = 26$ remainder 7
- $26/8 = 3$ remainder 2
- $3/8 = 0$ remainder 3
- Therefore, $(215)_{10} = (327)_8$

For 59:

- Divide by 8 repeatedly: $59/8 = 7$ remainder 3
- $7/8 = 0$ remainder 7
- Therefore, $(59)_{10} = (73)_8$

Table: Number Conversion Summary

Decimal	Binary	Octal
215	11010111	327
59	111011	73

Mnemonic: "Divide by base, read remainders bottom-up"

Question 1(c)(I) [2 marks]

Write the base of decimal, binary, octal and hexadecimal number system

Answer:

Table: Number System Bases

Number System	Base
Decimal	10
Binary	2
Octal	8
Hexadecimal	16

Mnemonic: "D-B-O-H: 10-2-8-16"

Question 1(c)(II) [2 marks]

$$(147)_{10} = (\quad)_2 = (\quad)_{16}$$

Answer:

Decimal to Binary conversion:

- $147/2 = 73$ remainder 1
- $73/2 = 36$ remainder 1
- $36/2 = 18$ remainder 0
- $18/2 = 9$ remainder 0
- $9/2 = 4$ remainder 1
- $4/2 = 2$ remainder 0
- $2/2 = 1$ remainder 0
- $1/2 = 0$ remainder 1
- Therefore, $(147)_{10} = (10010011)_2$

Decimal to Hexadecimal conversion:

- Group binary digits in sets of 4: 1001 0011
- Convert each group to hex: 1001 = 9, 0011 = 3
- Therefore, $(147)_{10} = (93)_{16}$

Table: Conversion Result

Decimal	Binary	Hexadecimal
147	10010011	93

Mnemonic: "Group by 4 from right for hex"

Question 1(c)(III) [3 marks]

Convert following binary code into grey code (i) 1011 (ii) 1110

Answer:

Binary to Gray code conversion procedure:

1. The MSB (leftmost bit) of the Gray code is the same as the MSB of the binary code
2. Other bits of the Gray code are obtained by XORing adjacent bits of the binary code

For 1011:

- MSB of Gray = MSB of Binary = 1
- Second bit = $1 \text{ XOR } 0 = 1$
- Third bit = $0 \text{ XOR } 1 = 1$
- Fourth bit = $1 \text{ XOR } 1 = 0$
- Therefore, $(1011)_2 = (1110)_{\text{Gray}}$

For 1110:

- MSB of Gray = MSB of Binary = 1
- Second bit = $1 \text{ XOR } 1 = 0$
- Third bit = $1 \text{ XOR } 1 = 0$
- Fourth bit = $1 \text{ XOR } 0 = 1$
- Therefore, $(1110)_2 = (1001)_{\text{Gray}}$

Table: Binary to Gray Code Conversion

Binary	Step-by-step	Gray Code
1011	$1, 1 \oplus 0 = 1, 0 \oplus 1 = 1, 1 \oplus 1 = 0$	1110
1110	$1, 1 \oplus 1 = 0, 1 \oplus 1 = 0, 1 \oplus 0 = 1$	1001

Mnemonic: "Keep first, XOR the rest"

Question 1(c) [OR Question] (I) [2 marks]

Write the full form of BCD and ASCII

Answer:

Table: Full Forms of BCD and ASCII

Abbreviation	Full Form
BCD	Binary Coded Decimal
ASCII	American Standard Code for Information Interchange

Mnemonic: "Binary Codes Decimal values, American Standards Code Information"

Question 1(c) [OR Question] (II) [2 marks]

Write 1's and 2's complement of following binary numbers: (i) 1010 (ii) 1011

Answer:

1's Complement: Invert all bits (change 0 to 1 and 1 to 0)

2's Complement: Take 1's complement and add 1

For 1010:

- 1's complement: 0101
- 2's complement: $0101 + 1 = 0110$

For 1011:

- 1's complement: 0100
- 2's complement: $0100 + 1 = 0101$

Table: Complement Results

Binary	1's Complement	2's Complement
1010	0101	0110
1011	0100	0101

Mnemonic: "Flip all bits for 1's, Add one more for 2's"

Question 1(c) [OR Question] (III) [3 marks]

Perform subtraction using 2's complement method (i) $(110110)_2 - (101010)_2$

Answer:

To subtract using 2's complement method:

1. Find 2's complement of subtrahend
2. Add it to the minuend
3. Discard any carry beyond the bit width

Subtraction: $(110110)_2 - (101010)_2$

Step 1: Find 2's complement of 101010

- 1's complement of 101010 = 010101
- 2's complement = $010101 + 1 = 010110$

Step 2: Add $110110 + 010110$

```

  1 1 1 1 1
  1 1 0 1 1 0
+ 0 1 0 1 1 0
-----
  0 0 1 1 0 0

```

Step 3: Result is $001100 = (12)_{10}$

Table: Subtraction Process

Step	Operation	Result
1	2's complement of 101010	010110
2	Add 110110 + 010110	001100
3	Final result (decimal)	12

Mnemonic: "Complement the subtracted, add them up, carry goes away"

Question 2(a) [3 marks]

Draw logic circuit of AND, OR and NOT gate using NAND gate only

Answer:

AND gate using NAND gates:


- AND gate = NAND gate followed by NOT gate (NAND gate)

OR gate using NAND gates:

- OR gate = Apply NOT (NAND gate) to both inputs, then NAND those results

NOT gate using NAND gate:

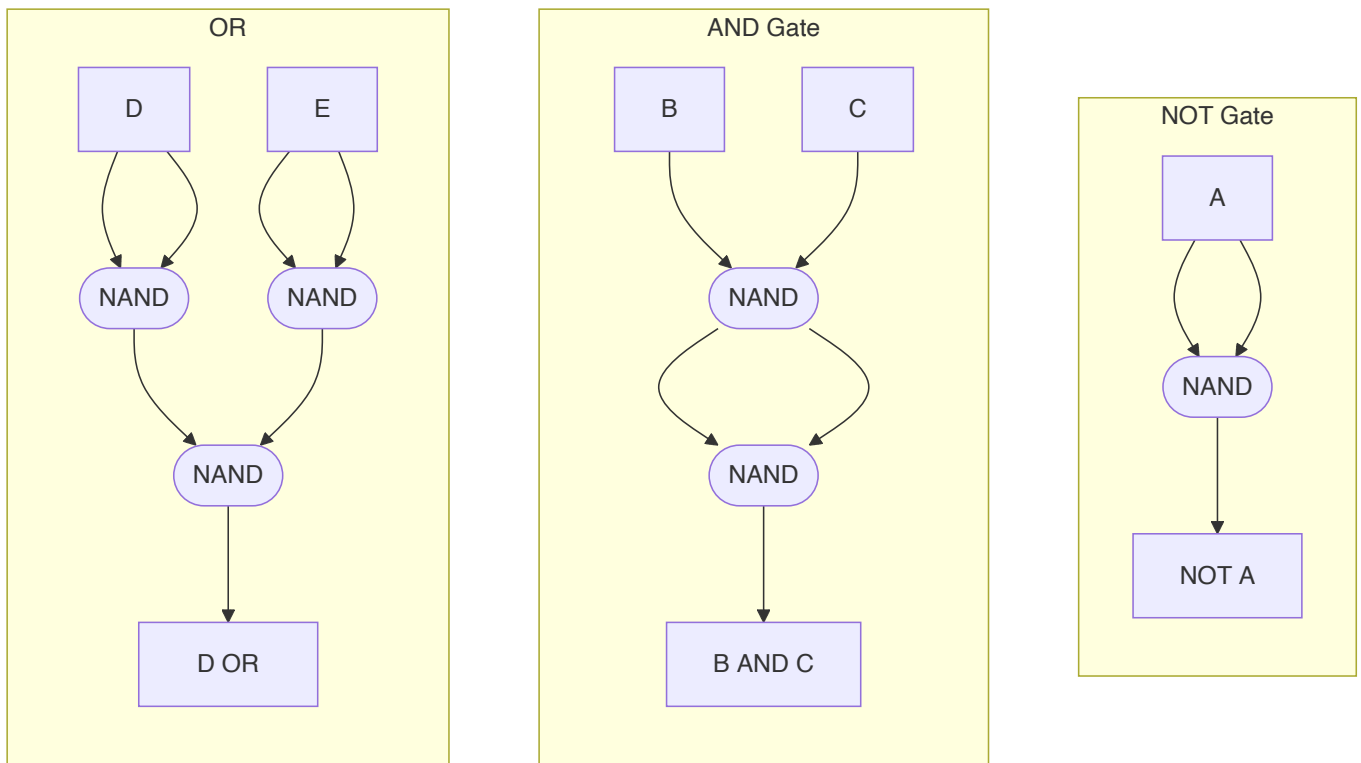- NOT gate = NAND gate with both inputs tied together



Mnemonic: "NAND alone for NOT, NAND twice for AND, NAND each then NAND again for OR"


Question 2(b) [4 marks]

Draw/Write logic symbol, truth table and equation of following logic gates (i) XOR gate (ii) OR gate

Answer:

XOR Gate:

Logic Symbol:

 


Truth Table:

A	B	Y (A⊕B)
0	0	0
0	1	1
1	0	1
1	1	0

Boolean Equation: $Y = A \oplus B = A'B + AB'$

OR Gate:

Logic Symbol:

 

Truth Table:

A	B	Y (A+B)
0	0	0
0	1	1
1	0	1
1	1	1

Boolean Equation: $Y = A + B$

Mnemonic: "XOR: Exclusive OR - one or the other but not both; OR: one or the other or both"

Question 2(c)(I) [3 marks]

Simplify the Boolean expression using algebraic method $Y = A + B[AC + (B + \bar{C})D]$

Answer:

Step-by-step simplification:

$$Y = A + B[AC + (B + \bar{C})D]$$

$$Y = A + B[AC + BD + \bar{C}D]$$

$$Y = A + BAC + BBD + B\bar{C}D$$

$$Y = A + BAC + BD + B\bar{C}D \quad (\text{Since } BB = B)$$

Apply absorption law ($X + XY = X$):

$$Y = A + AC + BD + B\bar{C}D \quad (\text{Since } A + BAC = A + AC)$$

$$Y = A + AC + BD + B\bar{C}D \quad (\text{Since } A + AC = A)$$

$$Y = A + B(D + \bar{C}D)$$

$$Y = A + BD + B\bar{C}D$$

$$Y = A + BD(1 + \bar{C})$$

$$Y = A + BD \quad (\text{Since } 1 + \bar{C} = 1)$$

Final expression: $Y = A + BD$

Table: Simplification Steps

Step	Expression	Law Applied
1	$A + B[AC + (B + \bar{C})D]$	Initial
2	$A + B[AC + BD + \bar{C}D]$	Distributive
3	$A + BAC + BBD + B\bar{C}D$	Distributive
4	$A + BAC + BD + B\bar{C}D$	Idempotent ($BB = B$)
5	$A + AC + BD + B\bar{C}D$	Absorption
6	$A + BD + B\bar{C}D$	Absorption ($A+AC=A$)
7	$A + B(D + \bar{C}D)$	Factoring
8	$A + BD$	Complementary law

Mnemonic: "Always look for idempotence, absorption, and complement patterns"

Question 2(c)(II) [4 marks]

Simplify the Boolean expression using Karnaugh Map $F(A,B,C) = \sum m(0, 2, 3, 4, 5, 6)$

Answer:

Create K-map for $F(A,B,C) = \sum m(0, 2, 3, 4, 5, 6)$:

K-map:

		BC			
		00	01	11	10
A	0	1	0	0	1
	1	1	1	0	1

Group the 1s:

- Group 1: m(0,4) - corresponds to $A'B'C'$
- Group 2: m(2,6) - corresponds to $B'C$
- Group 3: m(4,5) - corresponds to AB'

Simplified expression: $F(A,B,C) = B'C + A'B'C' + AB'$

Let's simplify further:


$$F(A,B,C) = B'C + B'C'(A' + A)$$

$$F(A,B,C) = B'C + B'C'$$

$$F(A,B,C) = B'(C + C')$$

$$F(A,B,C) = B'$$

Final expression: $F(A,B,C) = B'$

 Diagram: K-map grouping

Mnemonic: "Group adjacent 1s in powers of 2"

Question 2 [OR Question] (a) [3 marks]

Draw logic circuit of AND, OR and NOT gate using NOR gate only

Answer:

NOT gate using NOR gate:




- NOT gate = NOR gate with both inputs tied together

AND gate using NOR gates:

- AND gate = Apply NOT (NOR gate) to both inputs, then NOR those results again

OR gate using NOR gates:

   - OR gate = NOR gate followed by NOT gate (NOR gate)



Mnemonic: "NOR alone for NOT, NOT each then NOR for AND, Double NOR for OR"


Question 2 [OR Question] (b) [4 marks]

Draw/Write logic symbol, truth table and equation of following logic gates (i) NOR gate (ii) AND gate

Answer:

NOR Gate:

Logic Symbol:

 


Truth Table:

A	B	Y (A+B)'
0	0	1
0	1	0
1	0	0
1	1	0

Boolean Equation: $Y = (A+B)' = A'B'$

AND Gate:

Logic Symbol:

 

Truth Table:

A	B	Y (A·B)
0	0	0
0	1	0
1	0	0
1	1	1

Boolean Equation: $Y = A \cdot B$

Mnemonic: "NOR: NOT OR - neither one nor the other; AND: both must be 1"

Question 2 [OR Question] (c) [7 marks]

Write the Boolean expression of Q for above logic circuit. Simplify the Boolean expression of Q and draw the logic circuit of simplified circuit using AND-OR-Invert method

Answer:

Step 1: Write Boolean expression from the circuit:

$$Q = (A + B) \cdot (B + C \cdot ((B + C)'))$$

$$Q = (A + B) \cdot (B + C \cdot (B' \cdot C'))$$

$$Q = (A + B) \cdot (B + C \cdot B' \cdot C')$$

Step 2: Simplify the expression:

- Note that $C \cdot C' = 0$
- Therefore, $C \cdot B' \cdot C' = 0$
- So $Q = (A + B) \cdot (B + 0) = (A + B) \cdot B = A \cdot B + B \cdot B = A \cdot B + B = B + A \cdot B = B(1 + A) = B$

Step 3: Final simplified expression: $Q = B$

Step 4: AND-OR-Invert implementation of $Q = B$:

- This is simply a wire from input B to output Q

 


Table: Simplification Steps

Step	Expression	Simplification
1	$(A + B) \cdot (B + C \cdot ((B + C)'))$	Original expression
2	$(A + B) \cdot (B + C \cdot B' \cdot C')$	Applying De Morgan's
3	$(A + B) \cdot (B + 0)$	$C \cdot C' = 0$
4	$(A + B) \cdot B$	Simplifying
5	$A \cdot B + B \cdot B$	Distributive property
6	$A \cdot B + B$	Idempotent property ($B \cdot B = B$)
7	$B(1 + A)$	Factoring
8	B	$1 + A = 1$

Mnemonic: "When complementary variables multiply, they zero out"

Question 3(a) [3 marks]

Define combinational circuit. Give two examples of combinational circuits

Answer:

Combinational circuit: A digital circuit whose output depends only on the current input values and not on previous inputs or states. In combinational circuits, there is no memory or feedback.

Key characteristics:

- Output depends only on current inputs
- No memory elements
- No feedback paths

Examples of combinational circuits:

1. Multiplexers (MUX)
2. Decoders
3. Adders/Subtractors
4. Encoders
5. Comparators

Table: Combinational vs Sequential Circuits

Characteristic	Combinational Circuit	Sequential Circuit
Memory	No	Yes
Feedback	No	Usually
Output depends on	Current inputs only	Current and previous inputs
Examples	Multiplexers, Adders	Flip-flops, Counters

Mnemonic: "Combinational circuits: Current In, Current Out - no memory about"


Question 3(b) [4 marks]

Explain half adder using logic circuit and truth table

Answer:

Half Adder: A combinational circuit that adds two binary digits and produces sum and carry outputs.

Logic Circuit:

 

Truth Table:

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Boolean Equations:

- $\text{Sum} = A \oplus B = A'B + AB'$
- $\text{Carry} = A \cdot B$

Limitations:

- Cannot add three binary digits
- Cannot accommodate carry input from previous stage

Mnemonic: "XOR for Sum, AND for Carry"

Question 3(c)(I) [3 marks]

Explain multiplexer in brief**Answer:**

Multiplexer (MUX): A combinational circuit that selects one of several input signals and forwards it to a single output line based on select lines.


Key features:

- Acts as a digital switch
- Has 2^n data inputs, n select lines, and 1 output
- Select lines determine which input is connected to output

Common multiplexers:

- 2:1 MUX (1 select line)
- 4:1 MUX (2 select lines)
- 8:1 MUX (3 select lines)

Basic structure:

 **Applications:**

- Data routing
- Data selection
- Parallel to serial conversion
- Implementation of Boolean functions

Mnemonic: "Many In, Selection picks, One Out"

Question 3(c)(II) [4 marks]

Design 8:1 multiplexer. Write its truth table and draw its logic circuit

Answer:

8:1 Multiplexer Design:


- 8 data inputs (I_0 to I_7)
- 3 select lines (S_2, S_1, S_0)
- 1 output (Y)

Truth Table:

S_2	S_1	S_0	Output Y
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
1	0	0	I_4
1	0	1	I_5
1	1	0	I_6
1	1	1	I_7

Boolean Equation:

$$Y = S_2' \cdot S_1' \cdot S_0' \cdot I_0 + S_2' \cdot S_1' \cdot S_0 \cdot I_1 + S_2' \cdot S_1 \cdot S_0' \cdot I_2 + S_2' \cdot S_1 \cdot S_0 \cdot I_3 + S_2 \cdot S_1' \cdot S_0' \cdot I_4 + S_2 \cdot S_1' \cdot S_0 \cdot I_5 + S_2 \cdot S_1 \cdot S_0' \cdot I_6 + S_2 \cdot S_1 \cdot S_0 \cdot I_7$$

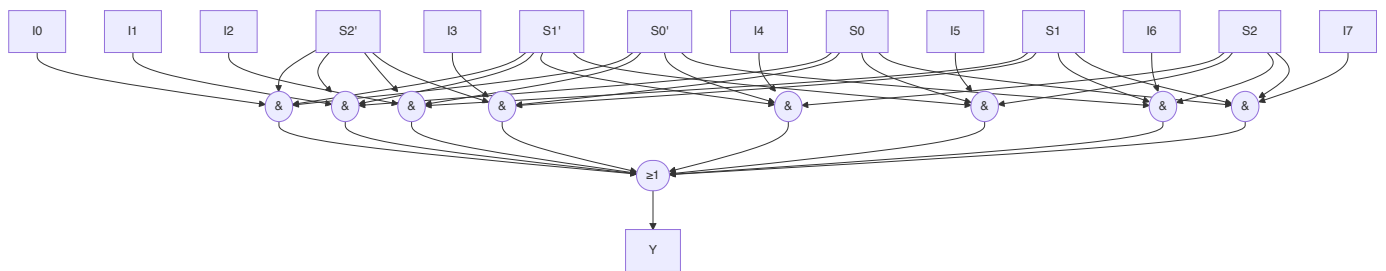Logic Circuit:

Mnemonic: "Eight inputs, three selects, decode and OR to output"


Question 3 [OR Question] (a) [3 marks]

Draw the block diagram of 4-bit binary parallel adder

Answer:

4-bit Binary Parallel Adder:

A circuit that adds two 4-bit binary numbers and produces a 4-bit sum and a carry output.

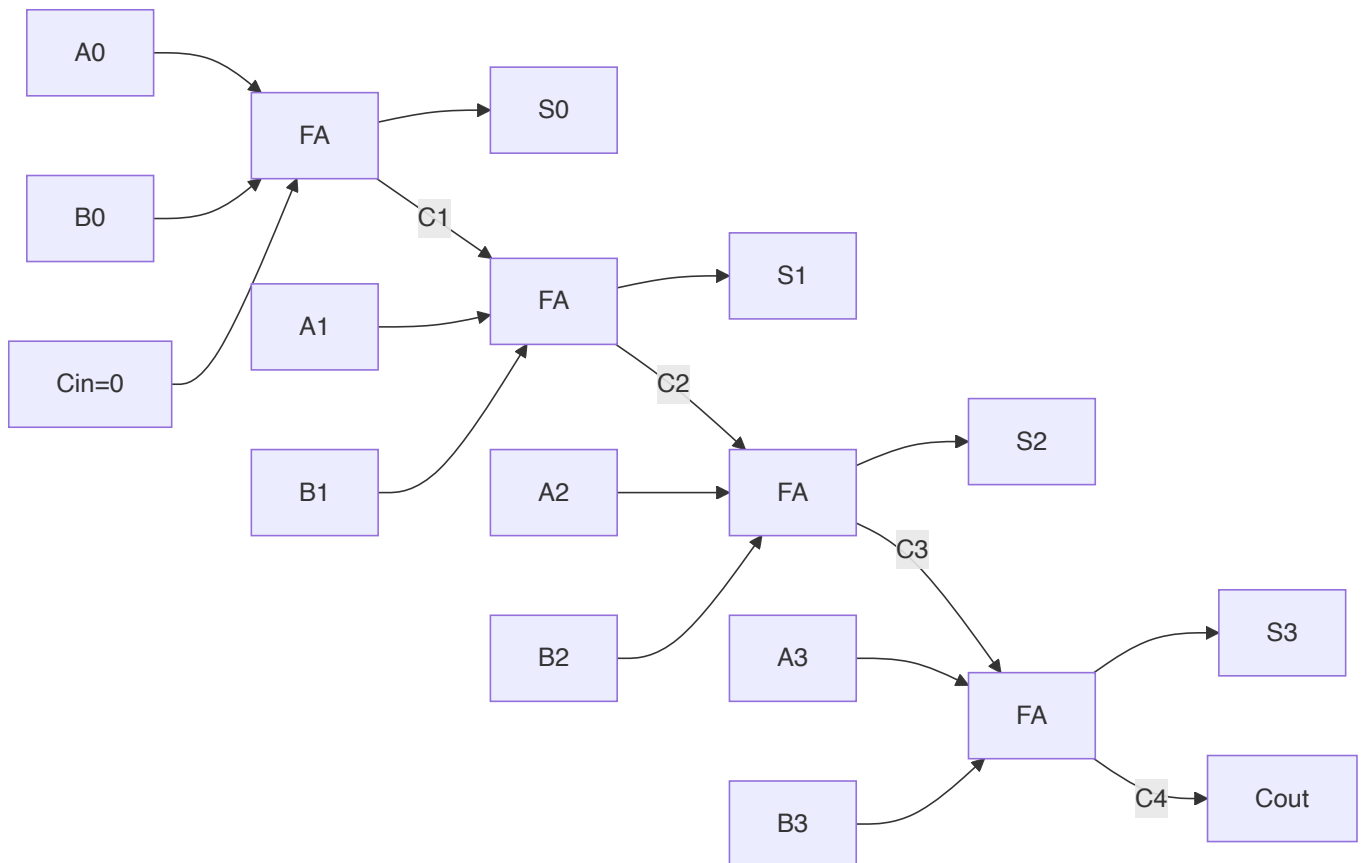**Components:**

- Four full adders (FA) connected in cascade
- Each FA adds corresponding bits and the carry from previous stage
- Initial carry-in (Cin) is typically 0

Mnemonic: "Four FAs linked, carries ripple through"


Question 3 [OR Question] (b) [4 marks]

Explain full adder using logic circuit and truth table

Answer:

Full Adder: A combinational circuit that adds three binary digits (two inputs and a carry-in) and produces sum and carry outputs.

Logic Circuit:

 

Truth Table:

A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Boolean Equations:

- $\text{Sum} = A \oplus B \oplus \text{Cin}$
- $\text{Cout} = A \cdot B + (A \oplus B) \cdot \text{Cin}$

Mnemonic: "XOR all three for Sum, OR the ANDs for Carry"


Question 3 [OR Question] (c) (I) [3 marks]

Explain 4:1 multiplexer using logic circuit and truth table

Answer:

4:1 Multiplexer: A digital switch that selects one of four input lines and connects it to the output based on two select lines.

Logic Circuit:

 

Truth Table:

S1	S0	Output Y
0	0	I0
0	1	I1
1	0	I2
1	1	I3

Boolean Equation:

$$Y = S1' \cdot S0' \cdot I0 + S1' \cdot S0 \cdot I1 + S1 \cdot S0' \cdot I2 + S1 \cdot S0 \cdot I3$$

Mnemonic: "Two select lines choose one of four inputs"

Question 3 [OR Question] (c) (II) [4 marks]


Design 8:1 multiplexer using two 4:1 multiplexer.

Answer:

Design approach: Use two 4:1 MUXes and one 2:1 MUX to create an 8:1 MUX.

1. First 4:1 MUX handles inputs I0-I3 using select lines S0,S1
2. Second 4:1 MUX handles inputs I4-I7 using select lines S0,S1
3. 2:1 MUX selects between outputs of the two 4:1 MUXes using S2

Block Diagram:

 

Truth Table:

S2	S1	S0	Output Y
0	0	0	I0
0	0	1	I1
0	1	0	I2
0	1	1	I3
1	0	0	I4
1	0	1	I5
1	1	0	I6
1	1	1	I7

Mnemonic: "S0,S1 select from each 4:1 MUX, S2 selects between them"

Question 4(a) [3 marks]

Define sequential circuit. Give two examples of it

Answer:

Sequential Circuit: A digital circuit whose output depends not only on the current inputs but also on the past sequence of inputs (history/previous states).

Key characteristics:

- Contains memory elements (flip-flops)
- Output depends on both current inputs and previous states
- Usually incorporates feedback paths
- Requires clock signals for synchronization (for synchronous circuits)

Examples of sequential circuits:

1. Flip-flops (SR, JK, D, T)
2. Registers (shift registers)
3. Counters (binary, decade, ring counters)
4. State machines
5. Memory units

Table: Sequential vs Combinational Circuits

Characteristic	Sequential Circuit	Combinational Circuit
Memory	Yes	No
Feedback	Usually	No
Output depends on	Current & previous inputs	Current inputs only
Clock required	Usually	No
Examples	Flip-flops, Counters	Multiplexers, Adders

Mnemonic: "Sequential remembers history, combinational only knows now"

Question 4(b) [4 marks]

Design decade counter

Answer:


Decade Counter: A sequential circuit that counts from 0 to 9 (decimal) and then resets to 0.

Design using JK flip-flops:

- Requires 4 JK flip-flops (Q3, Q2, Q1, Q0) to represent 4-bit binary number
- Counts from 0000 to 1001 (0-9 decimal) then resets

State Table:

Current State	Next State
0 (0000)	1 (0001)
1 (0001)	2 (0010)
2 (0010)	3 (0011)
3 (0011)	4 (0100)
4 (0100)	5 (0101)
5 (0101)	6 (0110)
6 (0110)	7 (0111)
7 (0111)	8 (1000)
8 (1000)	9 (1001)
9 (1001)	0 (0000)

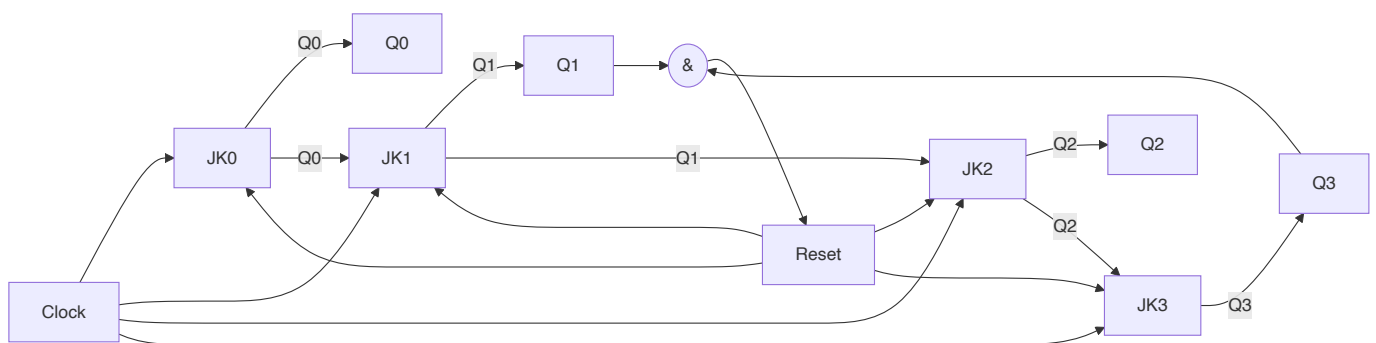Block Diagram:**J-K Input Equations:**

- $J_0 = K_0 = 1$ (toggle on every clock)
- $J_1 = K_1 = Q_0$
- $J_2 = K_2 = Q_1 \cdot Q_0$
- $J_3 = K_3 = Q_2 \cdot Q_1 \cdot Q_0$

Reset condition: When $Q_3 \cdot Q_1 = 1$ (state 1010), reset all flip-flops

Mnemonic: "Count BCD, reset after 9"


Question 4(c)(I) [3 marks]

Explain S-R flip-flop using NOR gate. Draw its logic symbol and write its truth table.


Answer:

S-R Flip-flop using NOR gates: A basic flip-flop constructed from two cross-coupled NOR gates that can store one bit of information.

Logic Circuit:

 

Logic Symbol:

 

Truth Table:

S	R	Q (next)	Q' (next)	Operation
0	0	Q (prev)	Q' (prev)	Memory (no change)
0	1	0	1	Reset
1	0	1	0	Set
1	1	0	0	Invalid (avoid)


Mnemonic: "S sets to 1, R resets to 0, both active gives invalid state"

Question 4(c)(II) [4 marks]

Explain S-R flip-flop using NAND gate. Write the limitation of SR flip flop

Answer:

S-R Flip-flop using NAND gates: A basic flip-flop constructed from two cross-coupled NAND gates.

 Logic Circuit:**Truth Table:**

S	R	Q (next)	Q' (next)	Operation
1	1	Q (prev)	Q' (prev)	Memory (no change)
1	0	1	0	Set
0	1	0	1	Reset
0	0	1	1	Invalid (avoid)

Limitations of SR Flip-flop:

1. **Invalid state:** When both $S=1$, $R=1$ (for NOR) or $S=0$, $R=0$ (for NAND), the output is unpredictable
2. **Race condition:** When inputs change simultaneously, the final state can be unpredictable
3. **No clocking mechanism:** Cannot synchronize with other digital components
4. **Not edge-triggered:** Cannot respond to brief pulses reliably
5. **Unwanted toggling:** May respond to noise or glitches

Table: NAND vs NOR SR Flip-flop

Characteristic	NAND SR Flip-flop	NOR SR Flip-flop
Active inputs	Low (0)	High (1)
Inactive inputs	High (1)	Low (0)
Invalid state	$S=0$, $R=0$	$S=1$, $R=1$

Mnemonic: "NAND: active-low inputs, NOR: active-high inputs; both have an invalid state"

Question 4 [OR Question] (a) [3 marks]

Write the definition of flip-flop. List the types of flip-flops

Answer:

Flip-flop: A basic sequential digital circuit that can store one bit of information and has two stable states (0 or 1). It serves as a basic memory element in digital systems.

Key characteristics:

- Bistable multivibrator (two stable states)
- Can maintain its state indefinitely until directed to change
- Forms the basic building block for registers, counters, and memory circuits
- Can be triggered by clock signals (synchronous) or level changes (asynchronous)

Types of Flip-flops:

Flip-flop Type	Description
SR (Set-Reset)	The most basic flip-flop with set and reset inputs
JK	Improved version of SR that eliminates invalid state
D (Data)	Stores the value at input D, used for data storage
T (Toggle)	Changes state when triggered, useful for counters
Master-Slave	Two-stage flip-flop that prevents race conditions

Mnemonic: "Storing a Single Step: SR, JK, D, T"

Question 4 [OR Question] (b) [4 marks]

Design 3-bit ring counter**Answer:**


Ring Counter: A circular shift register where only one bit is set (1) and all others are reset (0). The single set bit "rotates" around the register when clocked.

Design using D flip-flops:

- Requires 3 D flip-flops for 3-bit counter
- Initial state: 100, then cycles through 010, 001, and back to 100

State Table:

Current State	Next State
100	010
010	001
001	100

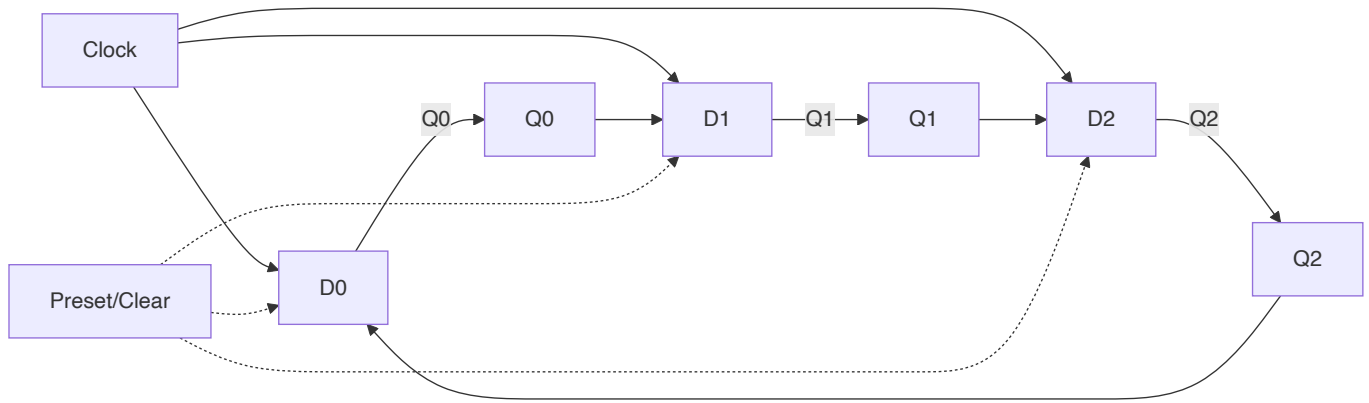Block Diagram:**D Input Equations:**

- $D0 = Q2$
- $D1 = Q0$
- $D2 = Q1$

Initial state setting: Preset FF0 to 1, Clear FF1 and FF2 to 0

Mnemonic: "One hot bit travels in a circle"


Question 4 [OR Question] (c)(I) [3 marks]

Explain J-K flip-flop using its logic symbol and truth table

Answer:

J-K Flip-flop: An improved version of SR flip-flop that eliminates the invalid state and provides predictable behavior in all input combinations.

Logic Symbol:

 

Truth Table:

J	K	Q (next)	Operation
0	0	Q (prev)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q' (prev)	Toggle

Key features:

- When J=K=1, the flip-flop toggles (changes to opposite state)
- No invalid state like in SR flip-flop
- Can perform all operations: Set, Reset, Hold, Toggle

Mnemonic: "J sets, K resets, Both toggle, None remember"

Question 4 [OR Question] (c)(II) [4 marks]

Draw logic circuit of D flip-flop and T flip-flop using J-K flip-flop


Answer:

D Flip-flop using JK Flip-flop:

To convert JK to D flip-flop:

- Connect D input to J
- Connect D' (NOT D) to K

Logic Circuit:

 


T Flip-flop using JK Flip-flop:

To convert JK to T flip-flop:

- Connect T input to both J and K

Logic Circuit:

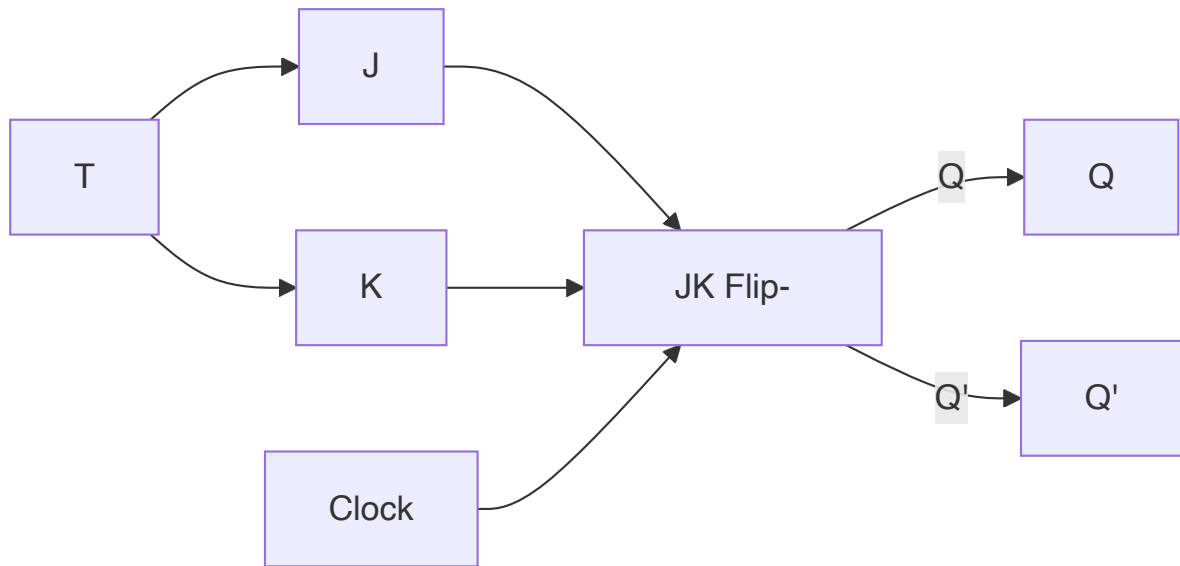

Truth Tables:

D Flip-flop:

D	Q (next)	Operation
0	0	Reset
1	1	Set

T Flip-flop:

T	Q (next)	Operation
0	Q (prev)	No change
1	Q' (prev)	Toggle

Mnemonic: "D directly follows, T toggles when true"

Question 5(a) [3 marks]

Compare RAM and ROM

Answer:

RAM (Random Access Memory) vs ROM (Read-Only Memory):

Table: RAM vs ROM Comparison

Characteristic	RAM	ROM
Full form	Random Access Memory	Read-Only Memory
Data retention	Volatile (loses data when power off)	Non-volatile (retains data without power)
Read/Write capability	Both read and write operations	Primarily read-only (except in PROM, EPROM, EEPROM)
Speed	Faster	Slower
Cost per bit	Higher	Lower
Applications	Temporary data storage, active program execution	Boot instructions, firmware, permanent data
Types	SRAM, DRAM	Mask ROM, PROM, EPROM, EEPROM, Flash
Cell complexity	More complex	Simpler

Mnemonic: "RAM Reads And Modifies (but forgets), ROM Remembers On shutdown (but fixed)"

Question 5(b) [4 marks]

Explain Serial In Serial Out shift register


Answer:


Serial In Serial Out (SISO) Shift Register: A sequential circuit that shifts data one bit at a time both at input and output.

Operation:

- Data enters serially one bit at a time
- Each bit shifts through the register on each clock pulse
- Data exits serially one bit at a time
- First-in, first-out operation

Block Diagram:

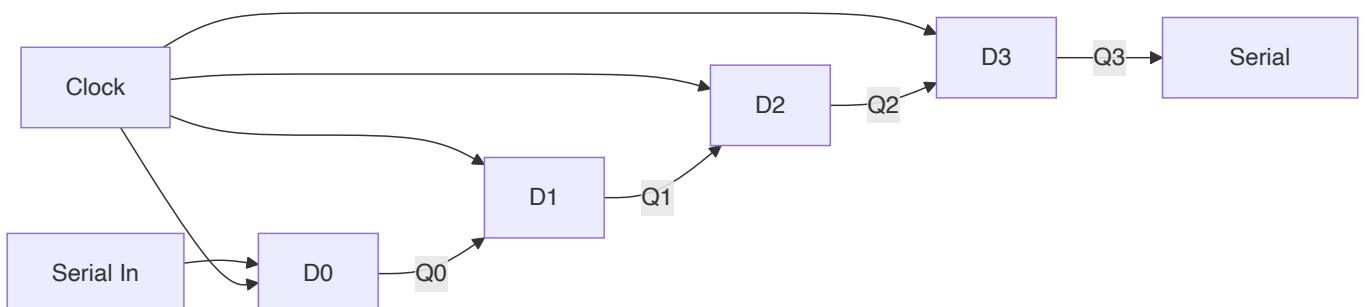

 Timing Diagram for shifting "1011":**Applications:**

- Data transmission between digital systems
- Serial-to-serial data conversion
- Time delay circuits
- Signal filtering

Mnemonic: "Bits enter line, march through chain, exit in sequence"

Question 5(c) [7 marks]**Write short note on logic families****Answer:**

Logic Families: Groups of digital integrated circuits with similar electrical characteristics, fabrication technology, and logic implementations.

Major Logic Families:**1. TTL (Transistor-Transistor Logic):**

- Based on bipolar junction transistors
- Standard series: 7400
- Supply voltage: 5V
- Moderate speed and power consumption
- High noise immunity
- Variants: Standard TTL, Low-power TTL (74L), Schottky TTL (74S), Advanced Schottky (74AS)

2. CMOS (Complementary Metal-Oxide-Semiconductor):

- Based on MOSFETs (P-type and N-type)
- Standard series: 4000, 74C00
- Wide supply voltage range (3-15V)
- Very low power consumption
- High noise immunity
- Susceptible to static electricity
- Advanced variants: HC, HCT, AC, ACT, AHC, AHCT series

3. ECL (Emitter-Coupled Logic):

- Based on differential amplifier with emitter-coupled transistors
- Extremely high speed (fastest logic family)
- High power consumption
- Low noise immunity
- Negative supply voltage
- Used in high-speed applications

Key Parameters of Logic Families:

Parameter	Description
Fan-in	Maximum number of inputs a gate can accept
Fan-out	Maximum number of gates that can be driven by one output
Noise margin	Ability to tolerate electrical noise
Propagation delay	Time delay between input and output transitions
Power dissipation	Power consumed by the gate
Figure of merit	Product of speed and power (lower is better)

Comparison Table:

Parameter	TTL	CMOS	ECL
Speed	Medium	Low to High	Very High
Power consumption	Medium	Very Low	High
Noise immunity	High	Very High	Low
Fan-out	10	50+	25
Supply voltage	5V	3-15V	-5.2V
Input/Output levels	0.8V/2.0V	30%/70% of VDD	-1.75V/-0.9V

Mnemonic: "TTL Takes Transistors, CMOS Conserves More Operational Supply, ECL Executes Calculations Lightning-fast"

Question 5 [OR Question] (a) [3 marks]**Compare SRAM and DRAM**

Answer:

SRAM (Static RAM) vs DRAM (Dynamic RAM):

Table: SRAM vs DRAM Comparison

Characteristic	SRAM	DRAM
Full form	Static Random Access Memory	Dynamic Random Access Memory
Cell structure	6 transistors (flip-flop)	1 transistor + 1 capacitor
Storage element	Flip-flop	Capacitor
Refreshing	Not required	Required periodically (ms)
Speed	Faster (access time: 10-30ns)	Slower (access time: 60-100ns)
Density	Lower (larger cell size)	Higher (smaller cell size)
Cost per bit	Higher	Lower
Power consumption	Higher	Lower
Applications	Cache memory, buffer	Main memory (RAM)
Data retention	As long as power is supplied	Few milliseconds, needs refresh

Mnemonic: "Static Stays steady with Six Transistors, Dynamic Drains and needs regular refreshing"

Question 5 [OR Question] (b) [4 marks]

Explain 8:3 encoder


Answer:

8:3 Encoder: A combinational circuit that converts 8 input lines to 3 output lines, essentially converting an active input line to its binary position.

Function:

- Has 8 input lines (I_0 to I_7) and 3 output lines (Y_2, Y_1, Y_0)
- Only one input is active at a time
- Output is the binary code representing position of active input

Logic Circuit:

 **Truth Table:**

Inputs	Outputs
$I_7 I_6 I_5 I_4 I_3 I_2 I_1 I_0$	$Y_2 Y_1 Y_0$
0 0 0 0 0 0 0 1	0 0 0
0 0 0 0 0 0 1 0	0 0 1
0 0 0 0 0 1 0 0	0 1 0
0 0 0 0 1 0 0 0	0 1 1
0 0 0 1 0 0 0 0	1 0 0
0 0 1 0 0 0 0 0	1 0 1
0 1 0 0 0 0 0 0	1 1 0
1 0 0 0 0 0 0 0	1 1 1

Boolean Equations:

- $Y_0 = I_1 + I_3 + I_5 + I_7$
- $Y_1 = I_2 + I_3 + I_6 + I_7$
- $Y_2 = I_4 + I_5 + I_6 + I_7$

Applications:

- Priority encoders
- Keyboard encoders
- Address decoders
- Data selectors

Mnemonic: "Eight Inputs become their position in Three bits"

Question 5 [OR Question] (c) [7 marks]

Define (i) Fan-in (ii) Fan-out (iii) Noise margin (iv) Propagation delay (v) Power dissipation for logic families

Answer:

Key Parameters of Logic Families:

1. Fan-in:

- **Definition:** Maximum number of inputs a logic gate can accept
- **Importance:** Determines complexity of logic implementation
- **Typical values:** 2-8 for most families
- **Example:** AND gate with 4 inputs has fan-in of 4

2. Fan-out:

- **Definition:** Maximum number of similar gates that one gate output can drive reliably
- **Importance:** Determines loading capability and system expandability
- **Calculation:** Based on output current capacity and input current requirements
- **Typical values:** TTL: 10, CMOS: 50+, ECL: 25

3. Noise Margin:

- **Definition:** Measure of circuit's ability to tolerate unwanted electrical noise/signals
- **Importance:** Ensures reliable operation in noisy environments
- **Calculation:** Difference between minimum high output voltage and maximum high input voltage
- **Typical values:** TTL: 0.4V, CMOS: 1.5V-2.25V, ECL: 0.2V

4. Propagation Delay:

- **Definition:** Time delay between input change and corresponding output change
- **Importance:** Determines maximum operating frequency and speed
- **Measurement:** Time from 50% of input transition to 50% of output transition
- **Typical values:** TTL: 10ns, CMOS: 5-100ns, ECL: 1-2ns


5. Power Dissipation:

- **Definition:** Amount of power consumed by a logic gate
- **Importance:** Affects heat generation, power supply requirements, battery life
- **Calculation:** Product of supply voltage and current drawn
- **Typical values:** TTL: 10mW, CMOS: 0.1mW (static), ECL: 25mW

Table: Logic Family Comparison

Parameter	TTL	CMOS	ECL
Fan-in	3-8	2-unlimited	2-4
Fan-out	10	50+	25
Noise margin	0.4V	1.5V-2.25V	0.2V
Propagation delay	10ns	5-100ns	1-2ns
Power dissipation	10mW	0.1mW (static)	25mW
Supply voltage	5V	3-15V	-5.2V
Figure of merit	100pj	10pj	50pj

Diagram: Noise Margin and Switching Thresholds

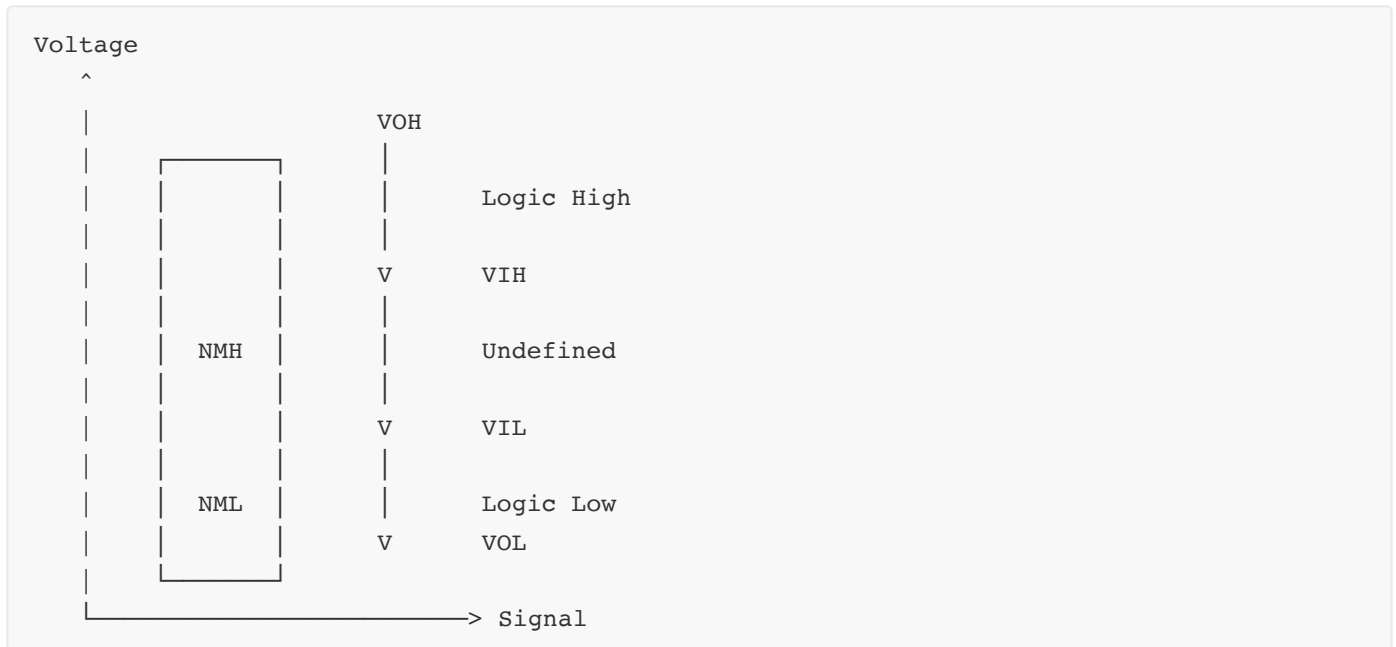

Relationships:

- NMH (Noise Margin High) = $V_{OH}(\min) - V_{IH}(\min)$
- NML (Noise Margin Low) = $V_{IL}(\max) - V_{OL}(\max)$
- Figure of Merit = Power \times Delay product (lower is better)

Mnemonic: "Five Factors: Fan-in counts inputs, Fan-out drives gates, Noise margin fights interference, Propagation delay measures speed, Power dissipation generates heat"