

Question 1(a) [3 marks]

What is negative feedback? List out advantages and disadvantages of negative feedback.

Answer:

Negative feedback is feeding a portion of output signal back to the input with 180° phase shift to reduce the input signal.

Advantages	Disadvantages
Increased stability	Reduced gain
Reduced distortion	Complex circuit design
Increased bandwidth	More components required
Reduced noise	Higher power consumption

Mnemonic: "SIRS" - Stability Improved, Reduced distortion, Sensitivity decreased


Question 1(b) [4 marks]

Describe the effect of negative feedback on frequency response and distortion of an amplifier.

Answer:

Negative feedback improves both frequency response and reduces distortion in amplifiers.

Diagram:

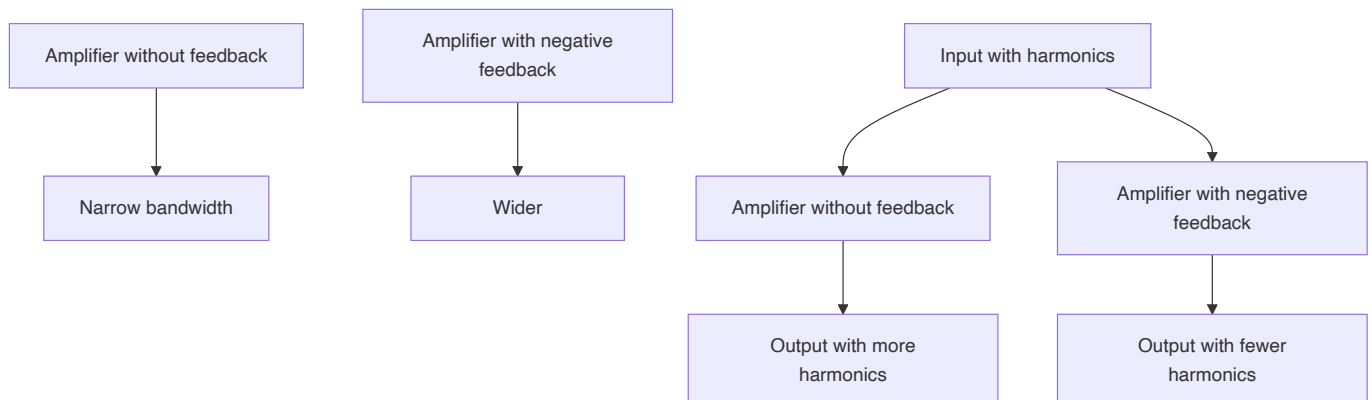

Effect on	Without feedback	With negative feedback
Frequency response	Narrow bandwidth	Wider bandwidth
Distortion	Higher harmonics	Reduced harmonics

Mnemonic: "WIDE" - With negative feedback, Improved response, Distortion reduced, Extended bandwidth


Question 1(c) [7 marks]

Derive an equation for overall gain of negative feedback voltage amplifier.

Answer:

The equation for overall gain of negative feedback voltage amplifier can be derived as follows:

Diagram:

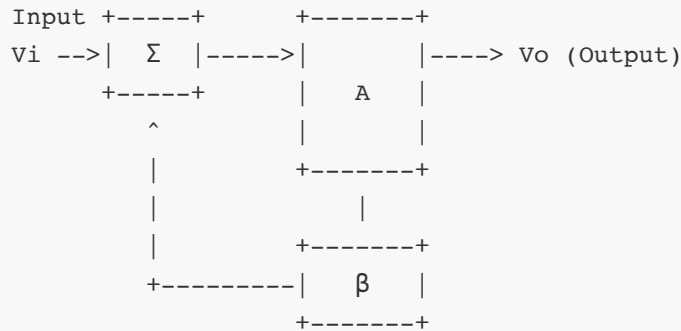

- **Input equation:** $V' = V_i - \beta V_o$
- **Output equation:** $V_o = AV'$
- **Substituting:** $V_o = A(V_i - \beta V_o)$
- **Solving for V_o :** $V_o = AV_i - A\beta V_o$
- **Rearranging:** $V_o(1 + A\beta) = AV_i$
- **Final equation:** $V_o/V_i = A/(1 + A\beta) = A_f$

Mnemonic: "LOOP" - Look at Original Open-loop gain and Proceed with feedback



Question 1(c) OR [7 marks]

Compare voltage shunt amplifier and current series amplifier.

Answer:

Parameter	Voltage Shunt Amplifier	Current Series Amplifier
Input	Voltage	Current
Output	Current	Voltage
Feedback network connection	Parallel at input	Series at input
Input impedance	Decreased	Increased
Output impedance	Increased	Decreased
Gain	Current gain decreases	Voltage gain decreases
Application	Current amplification	Voltage amplification

Diagram:

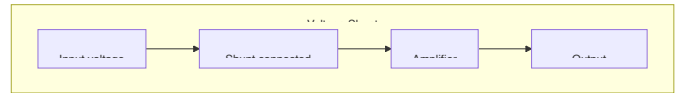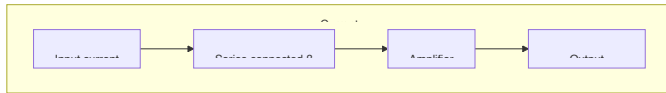

Mnemonic: "VICS" - Voltage shunt In, Current out Series has opposite

Question 2(a) [3 marks]


Discuss Barkhausen's criteria for oscillation.

Answer:

Barkhausen's criteria states that for sustained oscillations, the following conditions must be met:

Criteria	Requirement
Loop gain	$ A\beta = 1$ (magnitude equals 1)
Phase shift	Total phase shift around loop = 0° or 360°

Diagram:

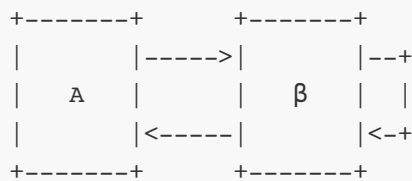


Mnemonic: "LOOP" - Loop gain One, Oscillation needs Phase shift zero


Question 2(b) [4 marks]

Draw circuit diagram of Hartley oscillator and Colpitts oscillator.


Answer:

Hartley Oscillator:

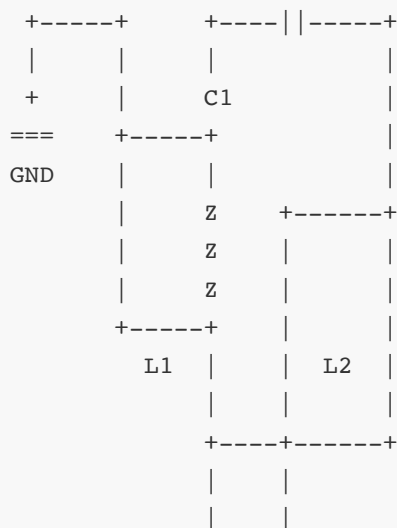

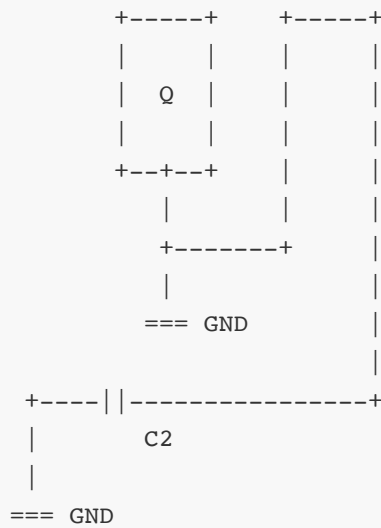

Colpitts Oscillator:

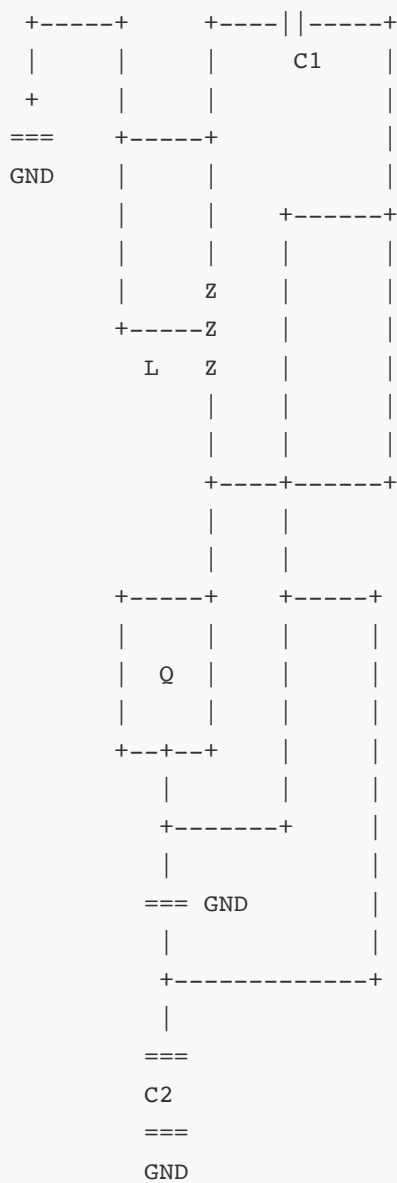

Mnemonic: "HaLs CoCs" - Hartley has inductors in series, Colpitts has Capacitors in series


Question 2(c) [7 marks]

Explain UJT as a relaxation oscillator.

Answer:

UJT (Unijunction Transistor) works as a relaxation oscillator by repeatedly charging and discharging a capacitor.

Diagram:

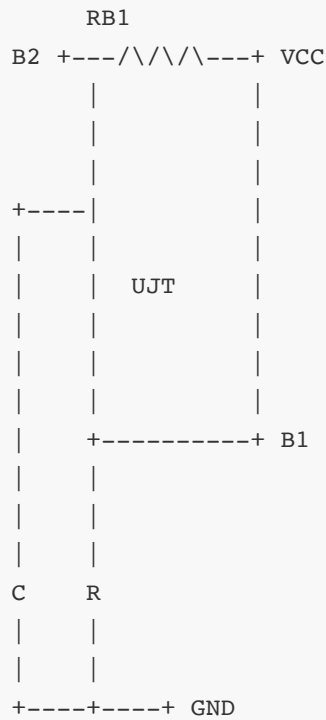

Phase	Description
Charging	Capacitor charges through R until voltage reaches VP (peak voltage)
Firing	UJT turns ON when emitter voltage reaches VP
Discharge	Capacitor discharges rapidly through UJT
Reset	Voltage falls below valley voltage, UJT turns OFF, cycle repeats

- **Intrinsic standoff ratio:** $\eta = RB1/(RB1+RB2)$
- **Peak voltage:** $VP = \eta \times VBB + VD$
- **Frequency:** $f = 1/[R \times C \times \ln(1/(1-\eta))]$

Mnemonic: "CFDR" - Charge, Fire, Discharge, Repeat


Question 2(a) OR [3 marks]

Classify Oscillators.

Answer:

Classification	Types
Based on feedback	RC, LC, Crystal
Based on waveform	Sinusoidal, Non-sinusoidal
Based on frequency	Audio, Radio, VHF, UHF
Based on circuit	Hartley, Colpitts, Wien-bridge, RC-phase shift

Diagram:

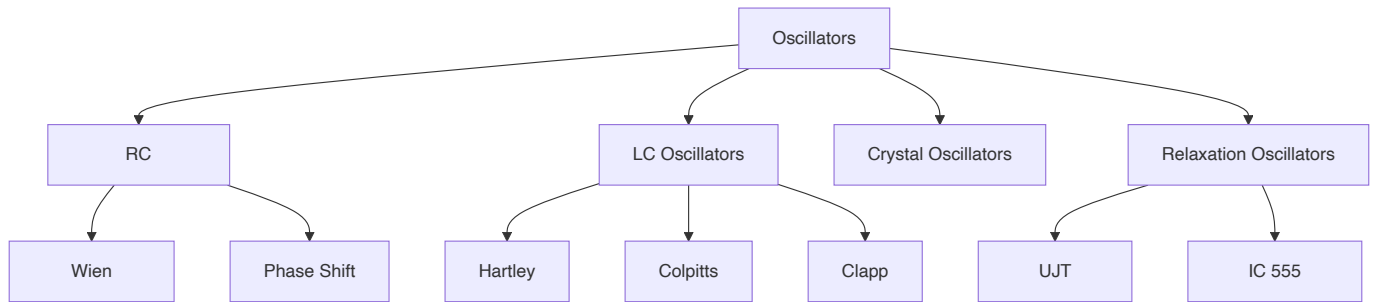

Mnemonic: "SRLC" - Sine waves from RC, LC, and Crystal oscillators

Question 2(b) OR [4 marks]


Explain construction of UJT with its symbol.

Answer:


UJT (Unijunction Transistor) consists of a lightly doped N-type silicon bar with electrical connections at both ends (bases) and a P-type emitter junction.


Diagram:

Symbol:

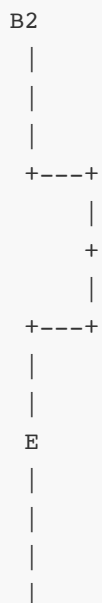

Structure:

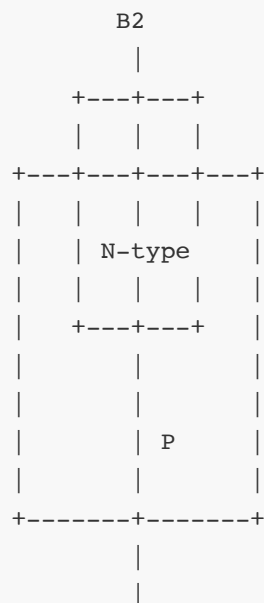

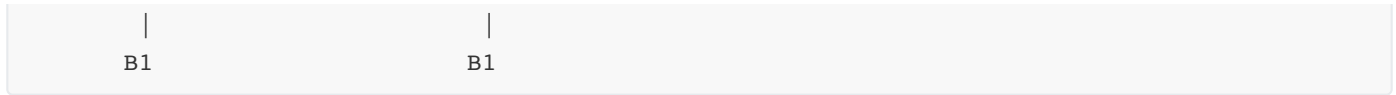

Component	Description
Base 1 (B1)	Connected to one end of N-type bar
Base 2 (B2)	Connected to other end of N-type bar
Emitter (E)	Connected to P-type region diffused into N-type bar
RB1	Resistance between emitter and B1
RB2	Resistance between emitter and B2

Mnemonic: "BEB" - Bases at Ends, Emitter in Between


Question 2(c) OR [7 marks]

Explain working of Wien Bridge oscillator circuit. List out its application.

Answer:

Wien Bridge oscillator produces sine waves using RC network for positive feedback and negative feedback for amplitude stability.

Diagram:

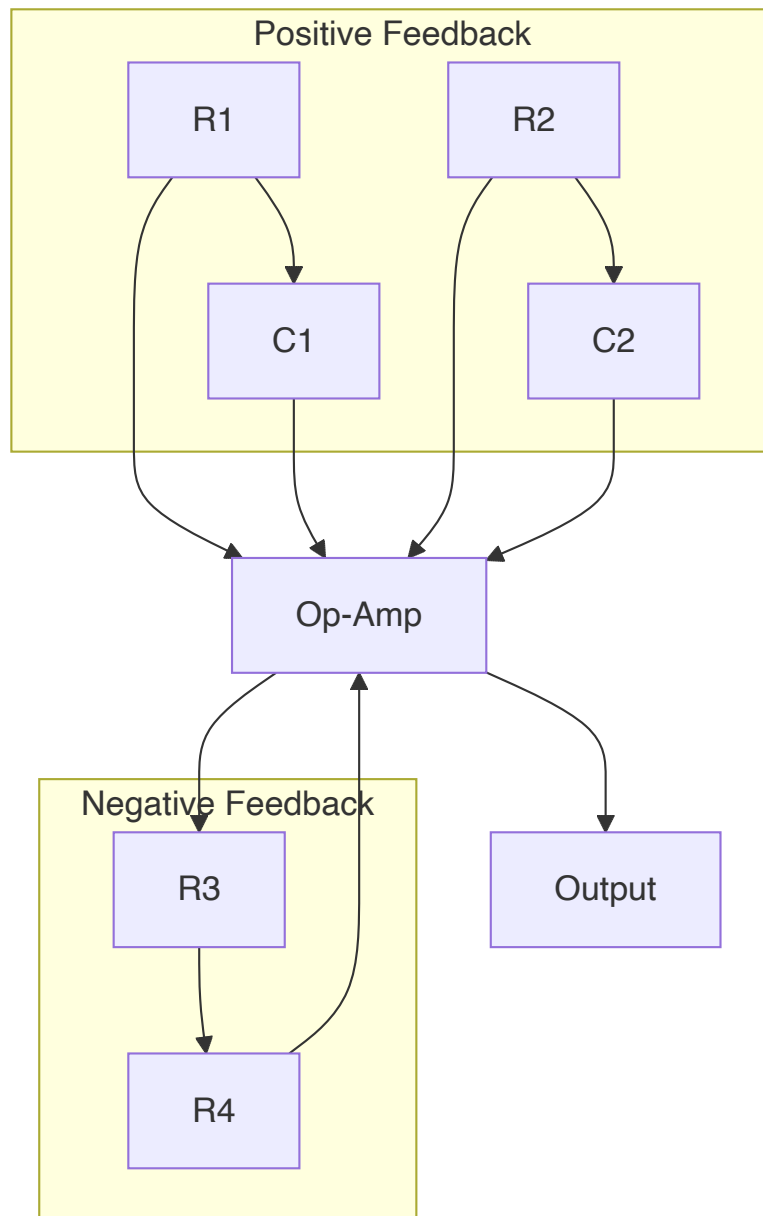

Component	Function
R1, C1 (series)	Positive feedback, phase lead
R2, C2 (parallel)	Positive feedback, phase lag
R3, R4	Negative feedback, amplitude control
Op-Amp	Active amplifier element

Applications:

- Audio signal generators
- Function generators
- Musical instrument tuning
- Test equipment

- Filter circuits

Mnemonic: "APPS" - Audio Production, Pure Sine waves, Stable frequency

Question 3(a) [3 marks]

Differentiate between voltage and power amplifier.

Answer:

Parameter	Voltage Amplifier	Power Amplifier
Primary function	Increases voltage level	Increases power level
Output	Low current capability	High current capability
Efficiency	Not critical	Critical parameter
Heat dissipation	Low	High, needs heat sink
Biasing	Class A typically	Class A, B, AB, or C
Applications	Pre-amplification stages	Driving speakers, motors

Mnemonic: "VICE" - Voltage amplifiers Increase voltage, Current not important, Efficiency not critical


Question 3(b) [4 marks]

Derive an equation for Efficiency of class B push pull amplifier.

Answer:

Efficiency (η) of a Class B push-pull amplifier is derived as follows:

Diagram:

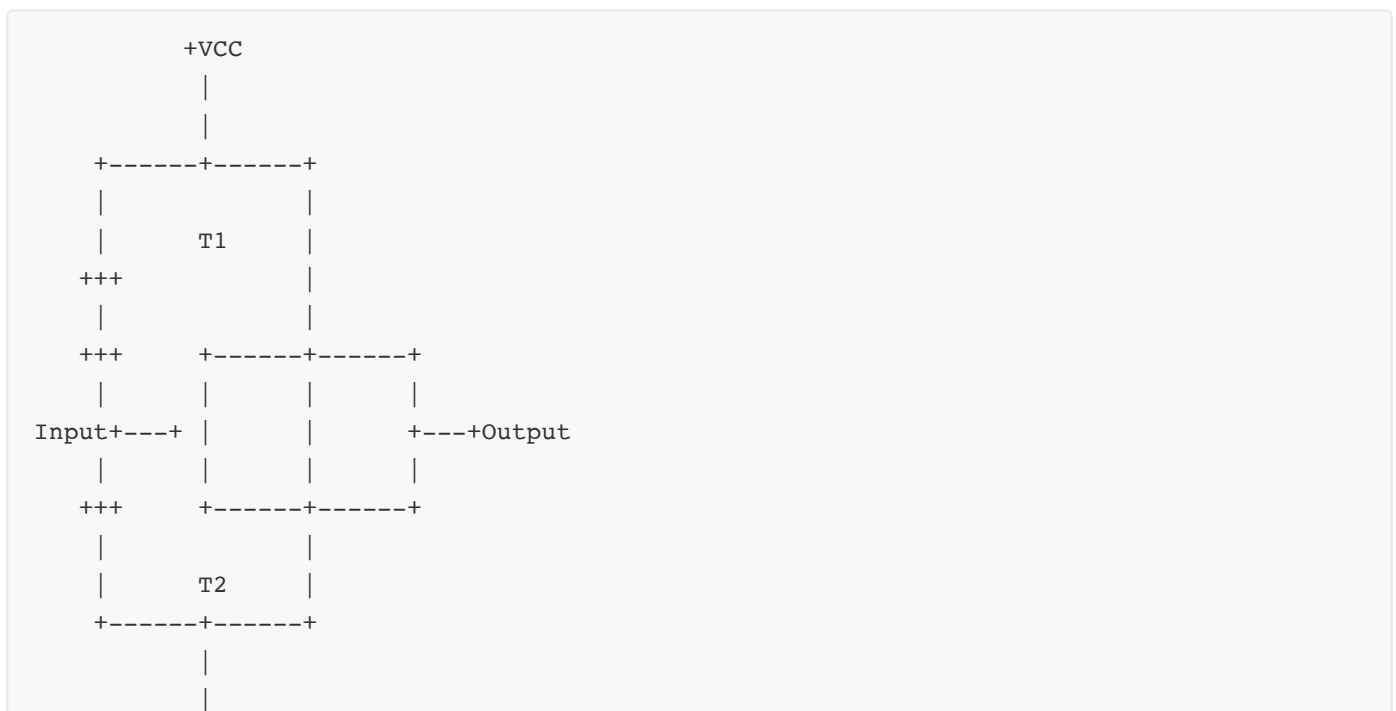

-VCC

- **AC power output:** $P_o = V_{rms} \times I_{rms} = (V_m/\sqrt{2}) \times (I_m/\sqrt{2}) = V_m \times I_m/2$
- **DC power input:** $P_{DC} = V_{CC} \times I_{DC} = V_{CC} \times (2 \times I_m/\pi)$
- **Efficiency:** $\eta = P_o/P_{DC} = (V_m \times I_m/2)/(V_{CC} \times 2 \times I_m/\pi) = (V_m \times \pi)/(4 \times V_{CC})$
- **For maximum swing:** $V_m = V_{CC}$, so $\eta = \pi/4 = 78.5\%$

Mnemonic: "POP" - Push-pull Output Power = $\pi/4$ or 78.5%


Question 3(c) [7 marks]

Explain working of Class-B Push Pull Amplifiers along with waveform.

Answer:

Class B push-pull amplifier uses two transistors to amplify opposite halves of the input waveform.

Diagram:

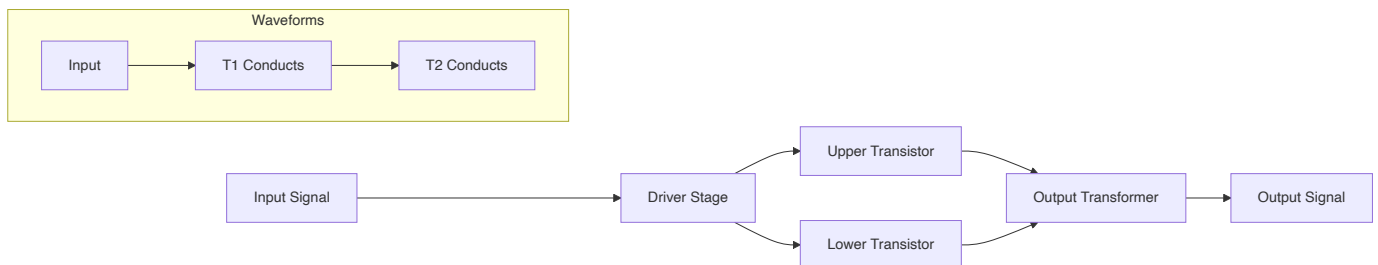

Phase	Description
Positive half	Upper transistor (T1) conducts, T2 is off
Negative half	Lower transistor (T2) conducts, T1 is off
Crossover	Both transistors are near cutoff, causing distortion

Key points:

- **Efficiency:** Approximately 78.5% ($\pi/4$)
- **Conduction angle:** 180° for each transistor
- **Crossover distortion:** Due to both transistors being off near zero crossing
- **Advantages:** Higher efficiency, less heat, suitable for high power

Mnemonic: "HOPE" - Half cycle Operation, Push-pull, Efficiency high


Question 3(a) OR [3 marks]

Explain Classification of Power amplifier.

Answer:

Class	Conduction Angle	Efficiency	Distortion
Class A	360°	25-30%	Low
Class B	180°	78.5%	Medium
Class AB	180°-360°	50-78.5%	Low-Medium
Class C	<180°	>78.5%	High

Diagram:

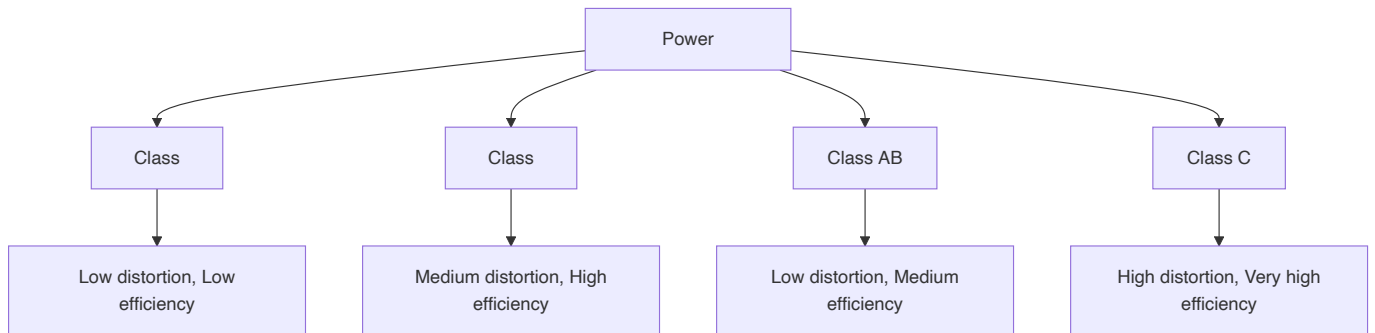

Mnemonic: "ABCE" - As Biasing Changes, Efficiency increases


Question 3(b) OR [4 marks]

Derive an equation for Efficiency of class A power amplifier.

Answer:

Efficiency of Class A power amplifier is derived as follows:

Diagram:

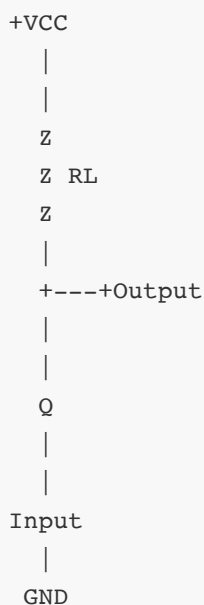

- **Maximum AC power output:** $P_o = (V_{rms})^2 / R_L = (V_{CC} / 2\sqrt{2})^2 / R_L = V_{CC}^2 / 8R_L$

- **DC power input:** $P_{DC} = V_{CC} \times I_{DC} = V_{CC} \times (V_{CC}/2R_L) = V_{CC}^2/2R_L$
- **Efficiency:** $\eta = P_o/P_{DC} = (V_{CC}^2/8R_L)/(V_{CC}^2/2R_L) = 1/4 = 25\%$

Mnemonic: "ONE" - Output Never Exceeds 25% efficiency in Class A


Question 3(c) OR [7 marks]

Explain working of Class-A transformer coupled Amplifiers along with waveform.

Answer:

Class A transformer coupled amplifier conducts for the full input cycle (360°) using a transformer for output coupling.

Diagram:

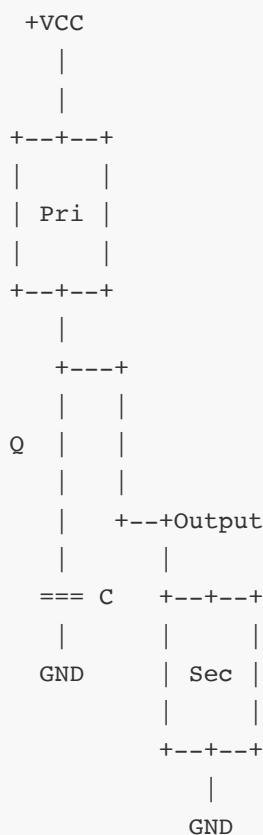

Component	Function
Transformer	Matches impedance, removes DC, provides isolation
Transistor	Conducts for full 360° cycle
Capacitor	AC coupling
VCC	DC power supply

Waveform characteristics:

- Input and output waveforms are in phase

Mnemonic: "FACT" - Full cycle Amplification in Class-a with Transformer

Question 4(a) [3 marks]

Define (i) CMRR (ii) Slew Rate

Answer:

Parameter	Definition	Typical Value
CMRR	Common Mode Rejection Ratio, the ratio of differential gain to common mode gain	90 dB (IC 741)
Slew Rate	Maximum rate of change of output voltage per unit of time	0.5 V/μs (IC 741)

CMRR: $CMRR = 20 \log_{10}(A_d/A_{cm})$ where A_d is differential gain and A_{cm} is common mode gain

Slew Rate: $SR = dV_{out}/dt$ (V/ μ s)

Mnemonic: "CRiSp" - CMRR Rejects common signals, Slew Rate limits speed


Question 4(b) [4 marks]

Explain inverting amplifier of operational amplifiers with sketch.

Answer:

Inverting amplifier provides gain with 180° phase shift using negative feedback.

Diagram:

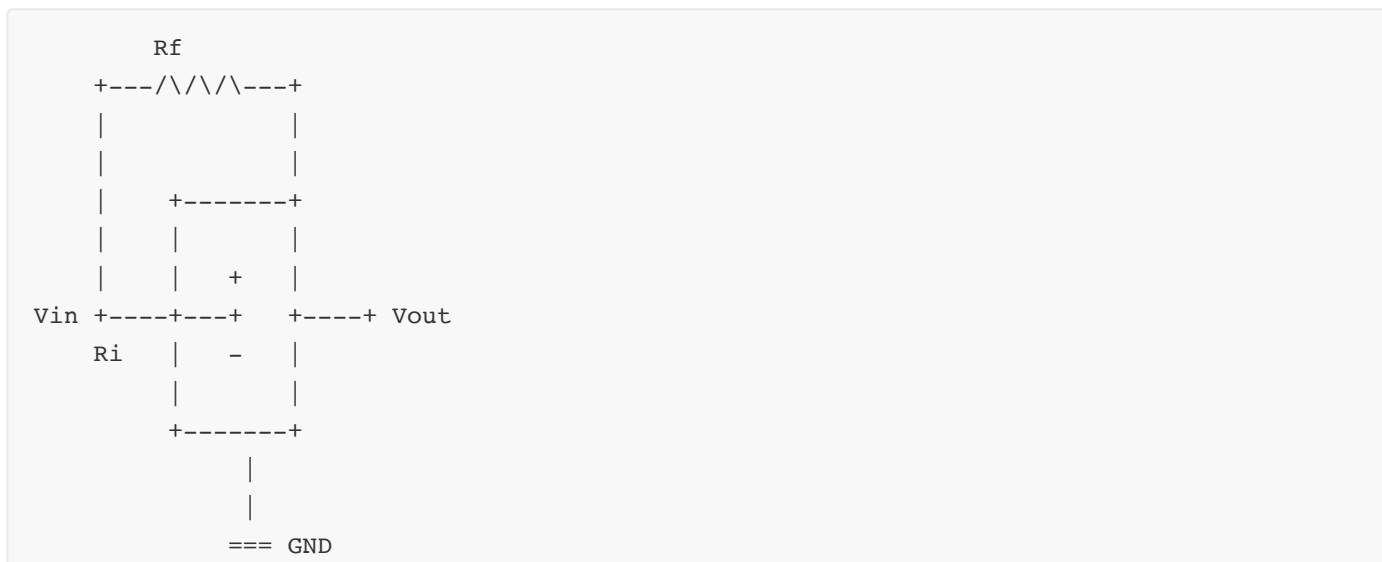

Component	Function
R_i	Input resistor
R_f	Feedback resistor
Op-Amp	Amplifies signal with high gain

Key equations:

- **Gain:** $A = -R_f/R_i$
- **Input impedance:** $Z = R_i$
- **Bandwidth:** Depends on op-amp and gain

Mnemonic: "IRON" - Inverting, Resistance ratio gives gain, Output Negative phase


Question 4(c) [7 marks]

Explain Op-amp as a Summing amplifier.


Answer:


Summing amplifier adds multiple input signals with weighted contributions.

Diagram:

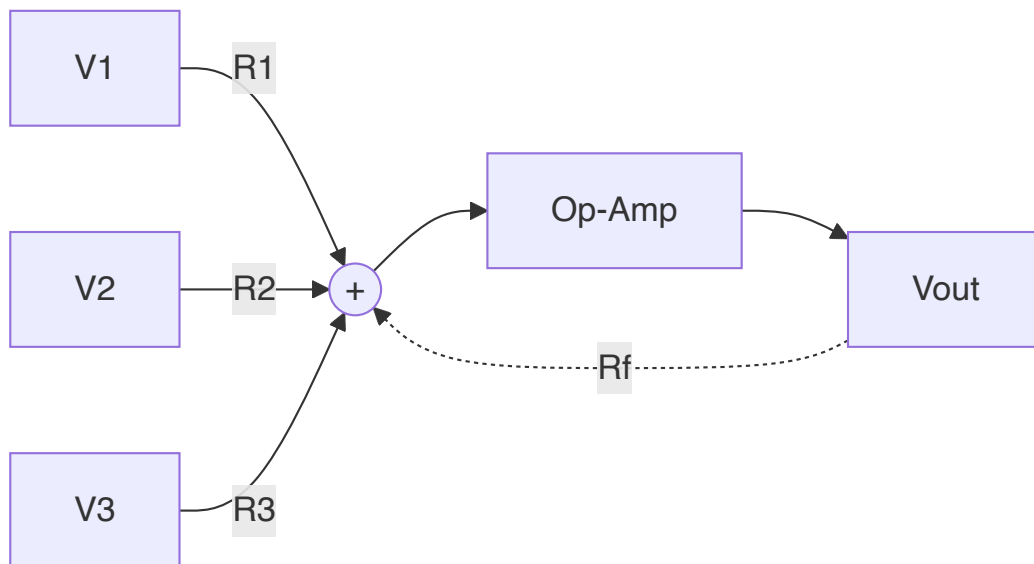

Circuit:

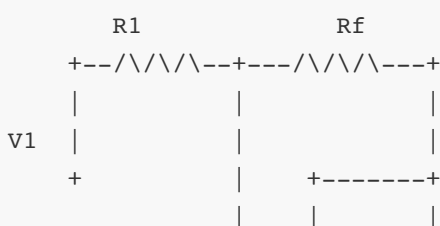

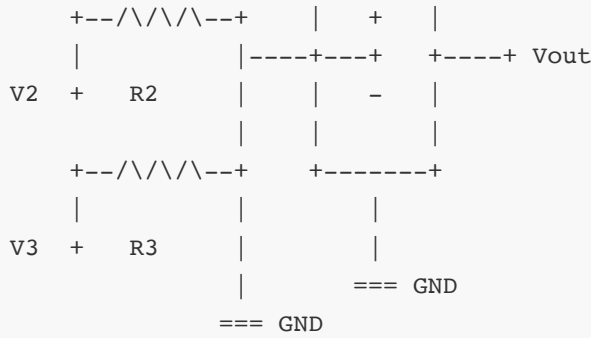

Parameter	Value
Output voltage	$V_{out} = -(R_f/R_1)V_1 - (R_f/R_2)V_2 - (R_f/R_3)V_3 \dots$
Gain for each input	$-R_f/R_n$ where R_n is input resistor
Equal weight summing	All input resistors equal: $R_1 = R_2 = R_3 = R_f$

Applications:

- Audio mixers
- Signal processing
- Analog computers
- Weighted averages


Mnemonic: "SARI" - Summing Amplifier Requires Inverting configuration

Question 4(a) OR [3 marks]

Sketch basic Block diagram of an operational amplifier.

Answer:

Diagram:

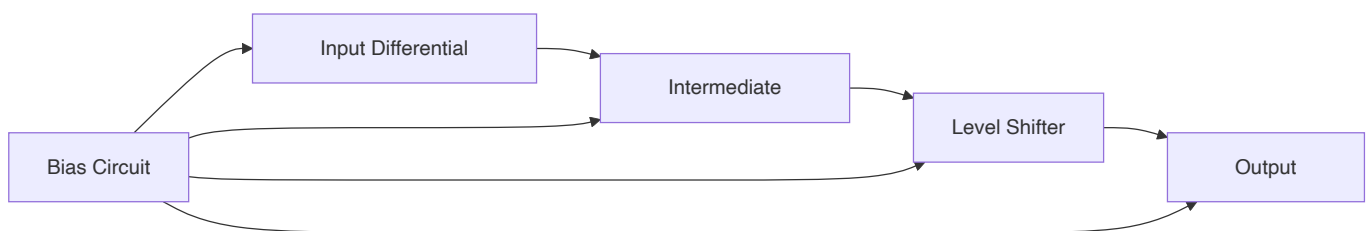

Stage	Function
Input differential stage	High input impedance, rejects common mode signals
Intermediate stage	High gain, frequency compensation
Level shifter	Shifts DC level for output stage
Output stage	Low output impedance, current amplification
Bias circuit	Provides proper operating points

Mnemonic: "DILO" - Differential Input, Level shifting, Output amplification


Question 4(b) OR [4 marks]

Explain non inverting amplifier of operational amplifiers with sketch.

Answer:

Non-inverting amplifier provides gain without phase inversion using negative feedback.

Diagram:

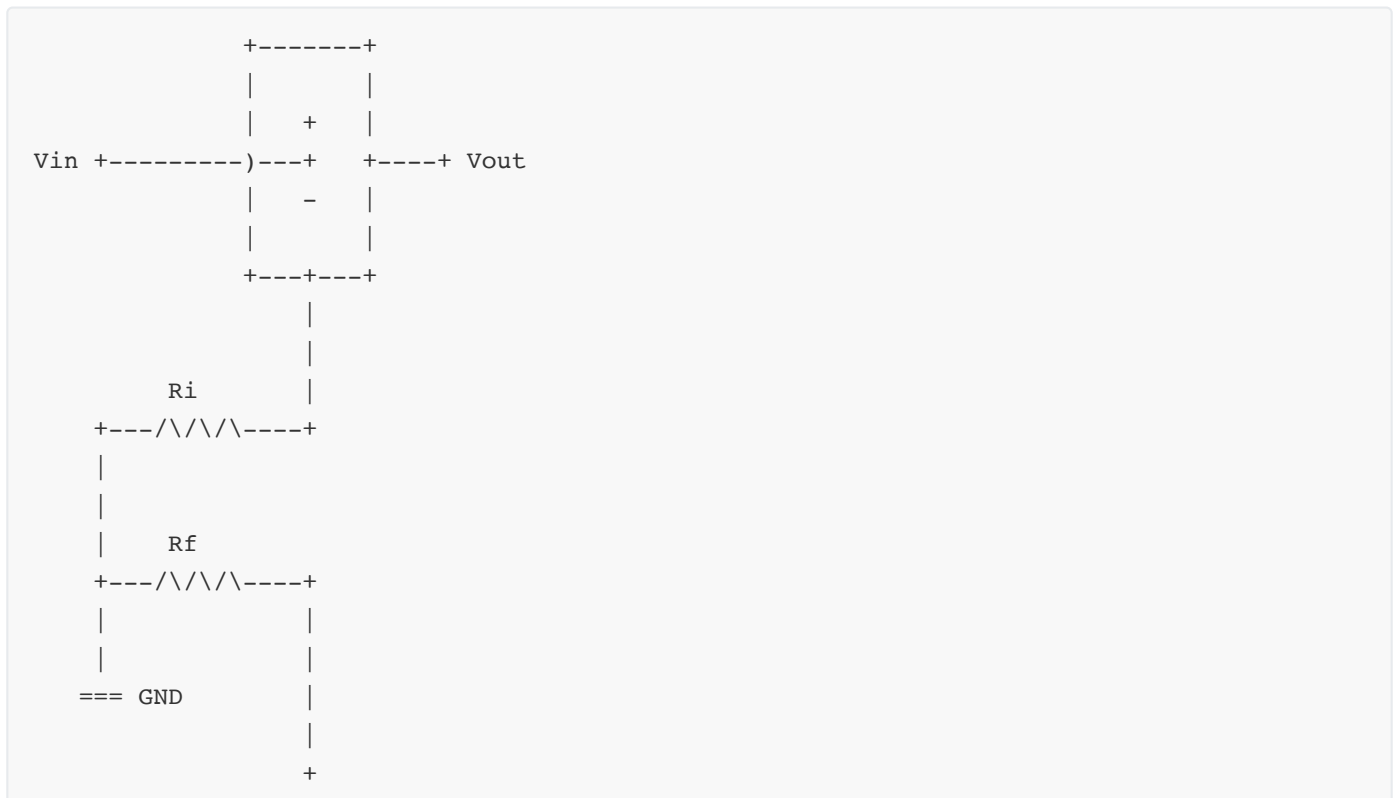

Parameter	Value
Gain	$A = 1 + R_f/R_i$
Input impedance	Very high (depends on op-amp)
Phase	In-phase with input
Common application	Voltage follower (when $R_f=0$, $R_i=\infty$)

Mnemonic: "NIPS" - Non-inverting, Input and output In Phase, Same polarity


Question 4(c) OR [7 marks]

Explain Op-amp as an Integrator.

Answer:

Op-amp integrator produces output proportional to the time integral of the input.

Diagram:

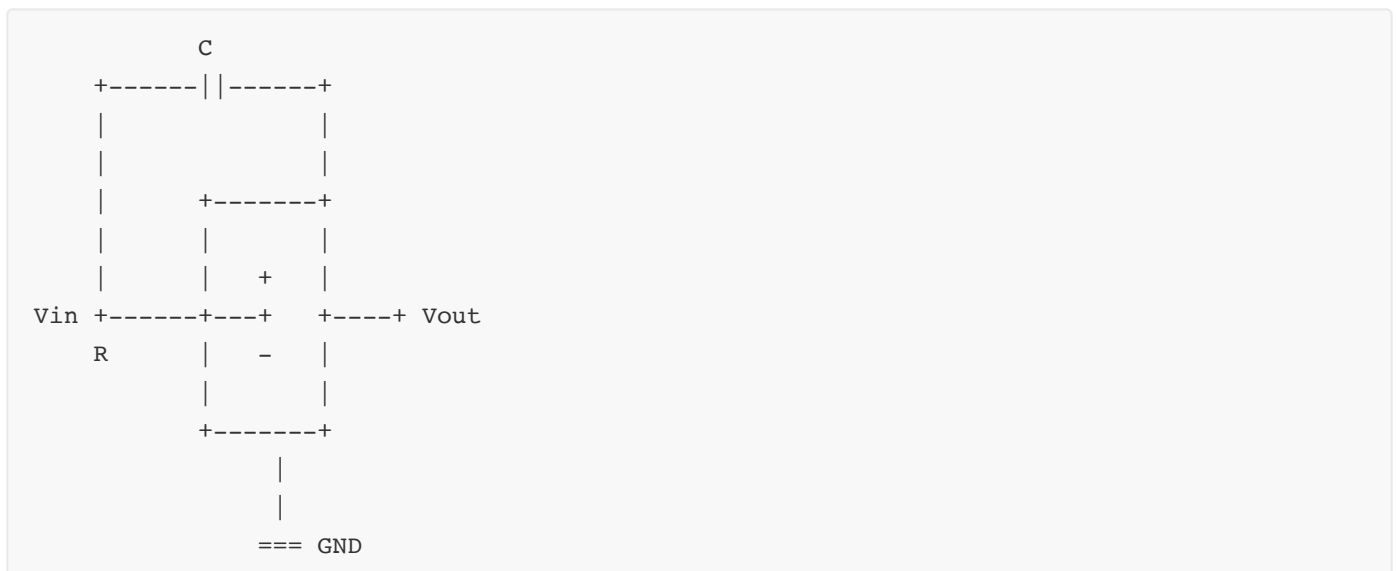

Parameter	Formula
Output voltage	$V_{out} = -(1/RC) \int V_{in} dt$
Transfer function	$V_{out}/V_{in} = -1/(sRC)$ in Laplace domain
Gain	Decreases at 20dB/decade with frequency
Phase shift	-90° (ideally)

Applications:

- Analog computers
- Waveform generators
- PID controllers

- Active filters
- Signal processing


Mnemonic: "TIME" - Takes Input and Makes time-dependent Effect

Question 5(a) [3 marks]

Draw Pin Diagram of IC 555.

Answer:

Diagram:

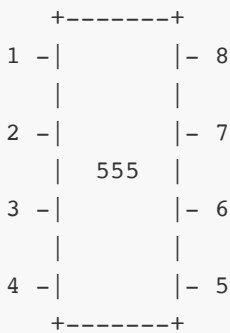

Pin Number	Name	Function
1	GND	Ground
2	TRIGGER	Starts timing cycle
3	OUTPUT	Timer output
4	RESET	Resets timer
5	CONTROL	Modifies timing
6	THRESHOLD	Ends timing cycle
7	DISCHARGE	Discharges timing capacitor
8	VCC	Positive supply

Mnemonic: "GTOR-CTD" - Ground, Trigger, Output, Reset, Control, Threshold, Discharge


Question 5(b) [4 marks]

Explain astable multivibrator of timer IC 555.

Answer:

Astable multivibrator using IC 555 generates continuous square wave output without any external trigger.

Diagram:

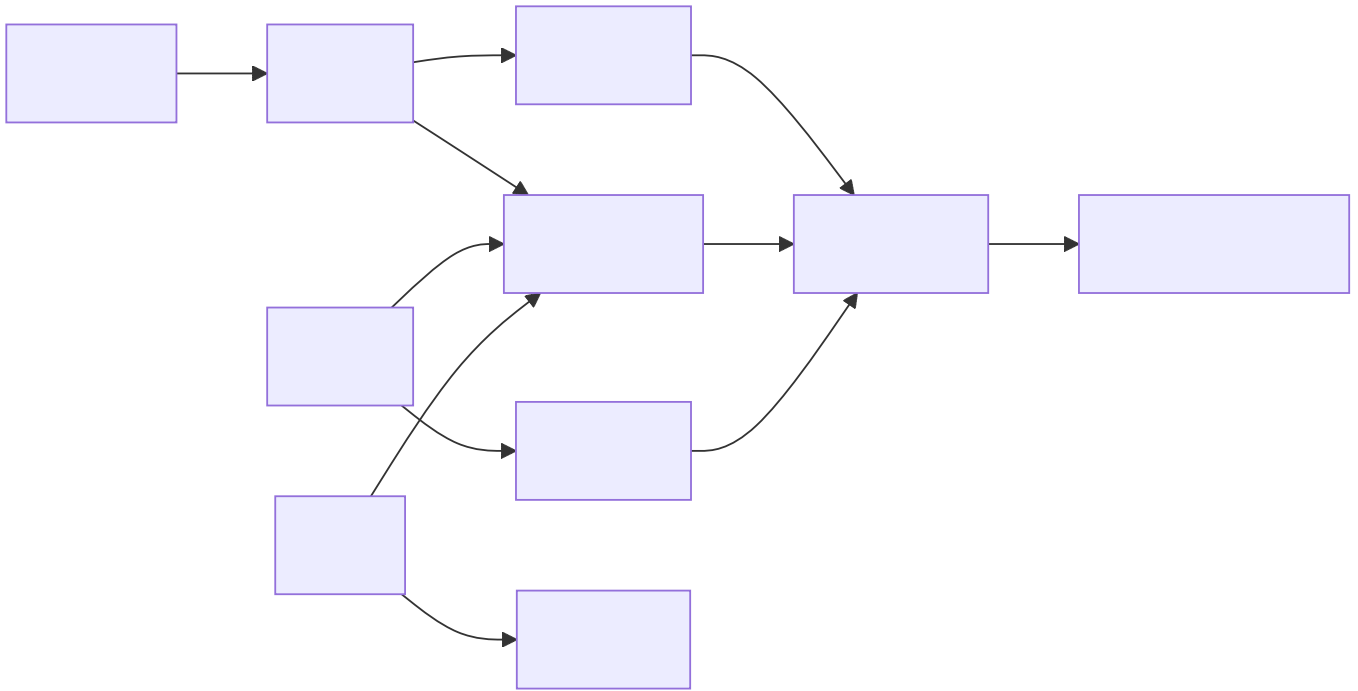

Parameter	Formula
Charging time	$t_1 = 0.693(R_1 + R_2)C$
Discharging time	$t_2 = 0.693(R_2)C$
Frequency	$f = 1.44 / ((R_1 + 2R_2)C)$
Duty cycle	$D = (R_1 + R_2) / (R_1 + 2R_2)$

Mnemonic: "FREE" - FREquency Established by External RC network


Question 5(c) [7 marks]


Explain working of Complementary symmetry Push Pull Amplifiers.

Answer:

Complementary symmetry push-pull amplifier uses complementary transistors (NPN and PNP) to amplify both halves of the waveform.

Diagram:

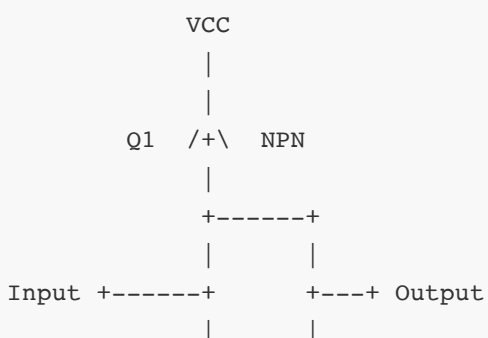

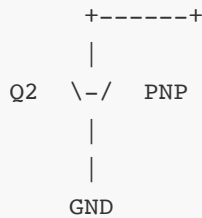

Transistor	Conduction	Current Flow
Q1 (NPN)	Positive half-cycle	Source to load
Q2 (PNP)	Negative half-cycle	Sink from load

Key features:

- **No center-tapped transformer:** Simpler design than transformer-coupled push-pull
- **Crossover distortion:** Requires biasing to minimize
- **Efficiency:** About 78.5% (Class B operation)
- **Thermal runaway:** Risk if not properly designed
- **Applications:** Audio power amplifiers, output stages of op-amps


Mnemonic: "COPS" - Complementary Opposing Pair of transistors for Symmetrical operation


Question 5(a) OR [3 marks]

Draw the diagram of Sequential Timer.

Answer:

Diagram:

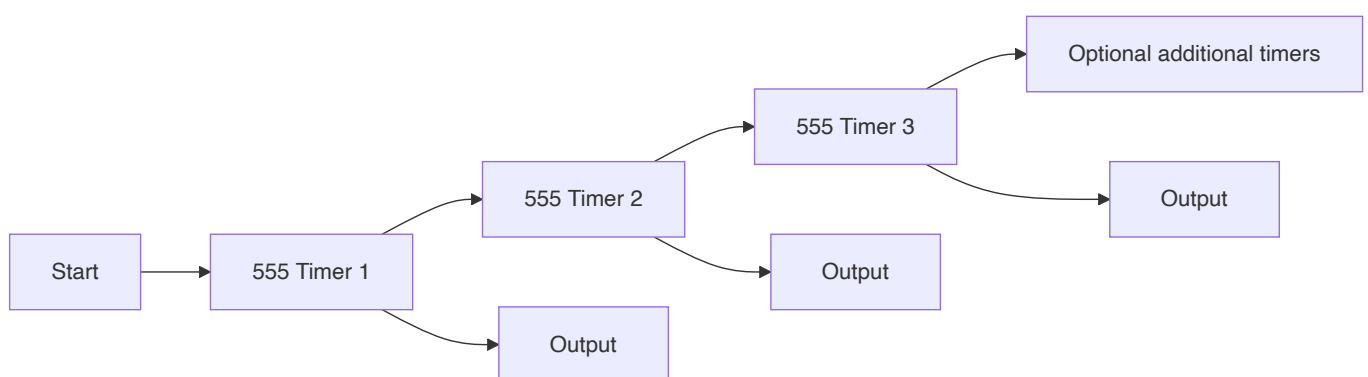

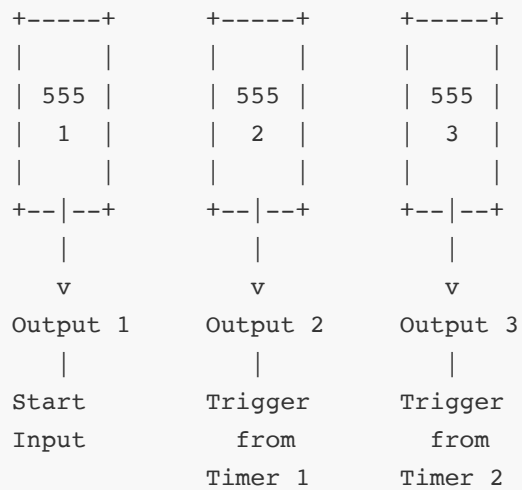

Mnemonic: "SET" - Sequential Events Triggered one after another


Question 5(b) OR [4 marks]

Explain bistable multivibrator of timer IC 555.

Answer:

Bistable multivibrator using IC 555 has two stable states and changes state only when triggered.

Diagram:

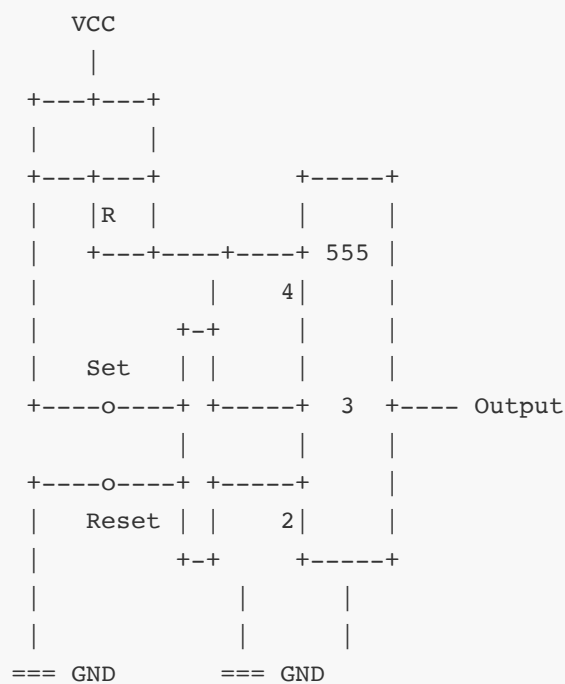

Terminal	Function	Operation
Pin 2 (TRIGGER)	SET input	When pulled below $1/3 V_{CC}$, output goes HIGH
Pin 4 (RESET)	RESET input	When pulled LOW, output goes LOW
Pin 3	Output	Remains in last state until triggered

Mnemonic: "FLIP" - Firmly Latched In Position until triggered


Question 5(c) OR [7 marks]

Compare different types of power Amplifiers.

Answer:

Parameter	Class A	Class B	Class AB	Class C
Conduction angle	360°	180°	180° - 360°	$<180^\circ$
Efficiency	25-30%	78.5%	50-78.5%	$>78.5\%$
Distortion	Very low	Moderate	Low	High
Biasing	Above cutoff	At cutoff	Slightly above cutoff	Below cutoff
Circuit complexity	Low	Medium	Medium	Low
Heat dissipation	High	Medium	Medium	Low
Applications	High fidelity audio	Audio power amps	Audio power amps	RF transmitters

Diagram:

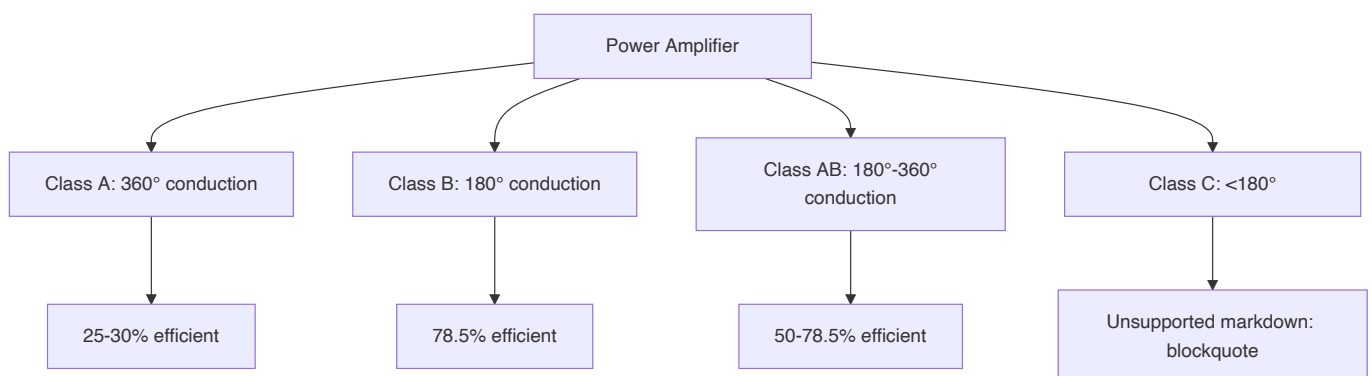

Mnemonic: "ABCE" - As Biasing Condition changes, Efficiency increases