


Question 1(a) [3 marks]

Explain the concept of dc load line with the help of neat diagram.

Answer:

DC load line is a straight line on output characteristics that shows all possible operating points of a transistor.

Diagram:

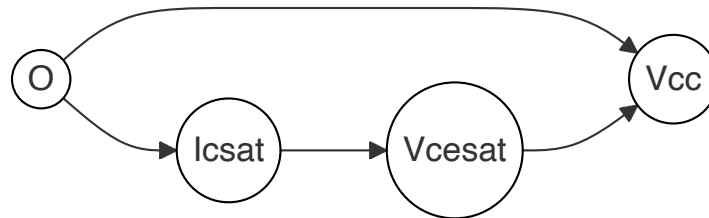

- **Collector saturation current:** When $V_{CE} = 0$, $I_C = V_{CC}/R_C$
- **Cutoff voltage:** When $I_C = 0$, $V_{CE} = V_{CC}$
- **Q-point:** Operating point along load line

Mnemonic: "LEVEL" - "Load line Establishes Voltage and current for Every Load condition"

Question 1(b) [4 marks]

Explain thermal runaway in detail.

Answer:

Thermal runaway is a condition where heat causes transistor's collector current to increase, which generates more heat, leading to destruction.

Diagram:



- **Heat generation:** Power dissipation = $V_{CE} \times I_C$
- **Critical effect:** Increased junction temperature decreases V_{BE}
- **Prevention:** Heat sinks, thermal stabilization circuits, proper biasing
- **Danger:** Can destroy transistor if not controlled



Mnemonic: "HEAT" - "Higher Emission Amplifies Temperature"

Question 1(c) [7 marks]

Draw the circuit diagram and frequency response of a two stage R-C coupled amplifier. Explain the importance of each component.

Answer:

R-C coupled amplifier uses capacitors to connect multiple transistor stages for higher gain.

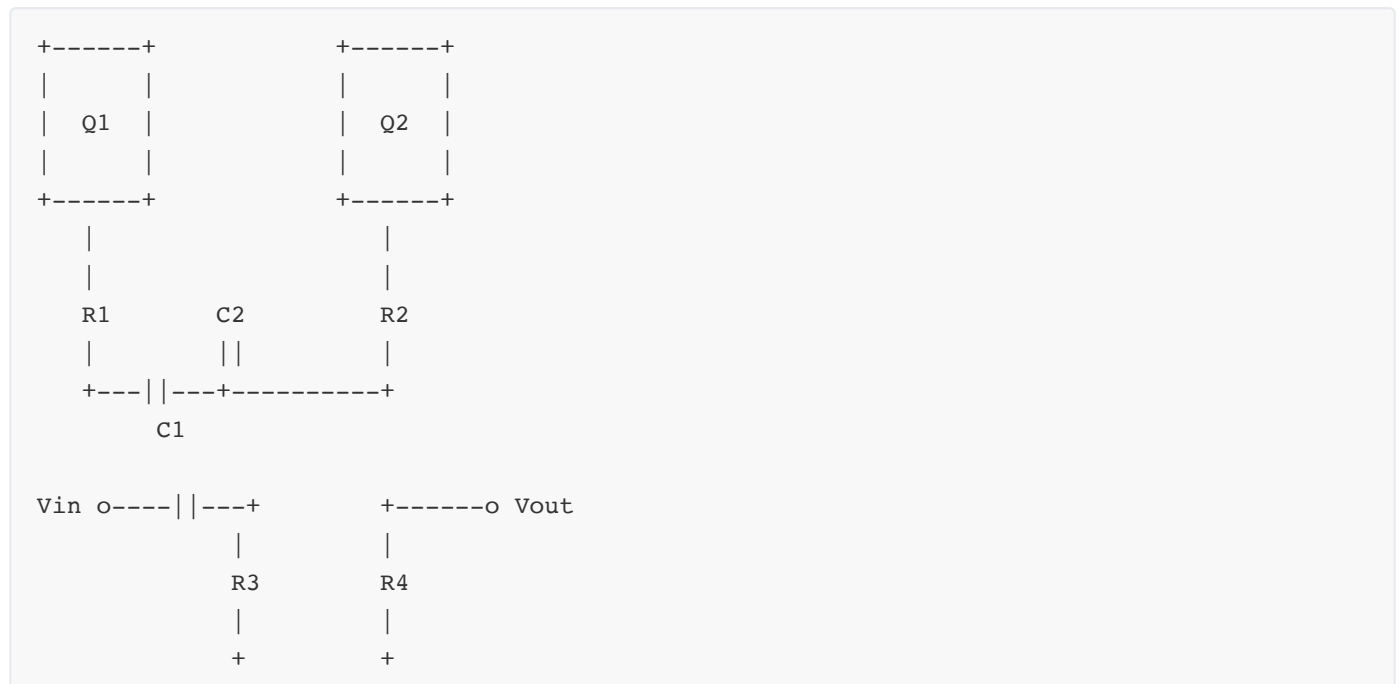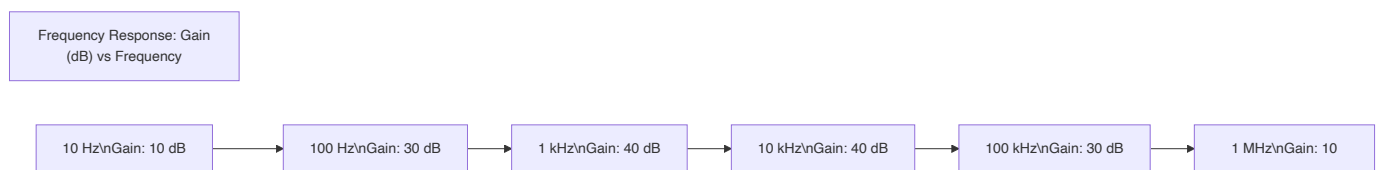Diagram:**Frequency Response:**

- **Coupling capacitors:** Block DC, allow AC signal transfer between stages
- **Biasing resistors:** Establish proper Q-point for transistor operation
- **Bypass capacitors:** Prevent gain reduction from negative feedback
- **Bandwidth:** Range between low and high cutoff frequencies

Mnemonic: "CARS" - "Coupling capacitors Allow Resistance Separation"

OR

Question 1(c) [7 marks]

Compare negative and positive feedback in amplifier.

Answer:

Feedback systems return a portion of output to the input with different effects based on polarity.

Table:

| Parameter | Negative Feedback | Positive Feedback |
|------------------------|------------------------|-------------------------------|
| Gain | Decreases | Increases |
| Bandwidth | Increases | Decreases |
| Stability | Improves | Decreases |
| Distortion | Reduces | Increases |
| Noise | Reduces | Amplifies |
| Input/Output impedance | Can be controlled | Unpredictable |
| Applications | Amplifiers, regulators | Oscillators, Schmitt triggers |

- **Negative feedback:** Output is out of phase with input (180° shifted)
- **Positive feedback:** Output is in phase with input (0° shifted)
- **Barkhausen criteria:** Positive feedback with unity gain creates oscillation

Mnemonic: "SIGN" - "Stability Increases with Gain Negation"


Question 2(a) [3 marks]

State and explain Barkhausen's criteria for oscillations.

Answer:

Barkhausen's criteria define conditions for sustained oscillations in a feedback system.

Diagram:

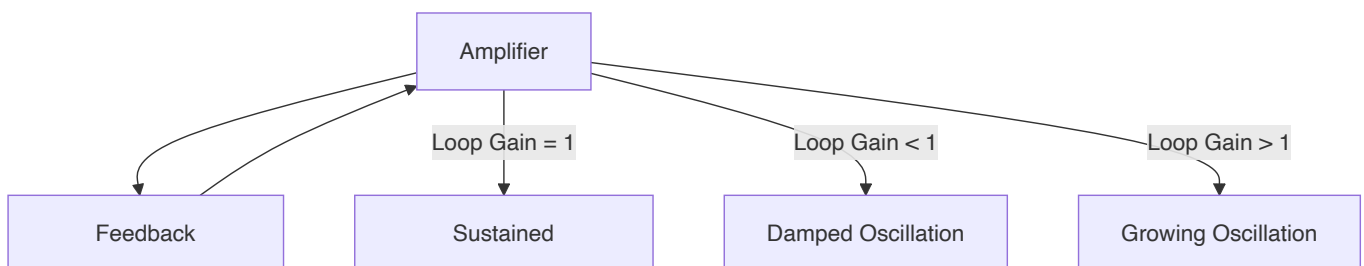

- **Gain condition:** Loop gain ($A \times \beta$) must equal 1 (unity)
- **Phase condition:** Total phase shift must be 0° or 360°
- **Practical implementation:** Initial loop gain > 1 , then stabilizes at 1

Mnemonic: "LOOP" - "Loop's Overall Output Phase"

Question 2(b) [4 marks]

Compare Fixed bias, Collector to base bias & Voltage divider bias methods.

Answer:

Different biasing techniques provide varying degrees of stability and temperature compensation.

Table:

| Parameter | Fixed Bias | Collector-Base Bias | Voltage Divider Bias |
|-----------------------|------------|---------------------|----------------------|
| Stability | Poor | Better | Excellent |
| Circuit complexity | Simple | Medium | Complex |
| Temperature stability | Poor | Medium | Good |
| Components | 1 Resistor | 1 Resistor | 3-4 Resistors |
| Stability factor (S) | High | Medium | Low |

- **Fixed bias:** Single resistor from base to VCC
- **Collector-base bias:** Feedback resistor from collector to base
- **Voltage divider:** Two resistors create stable reference voltage


Mnemonic: "STORM" - "Stability Through Optimized Resistor Methods"

Question 2(c) [7 marks]

Write short note on Hartley oscillator.

Answer:

Hartley oscillator is an LC oscillator with a tapped inductor for feedback.

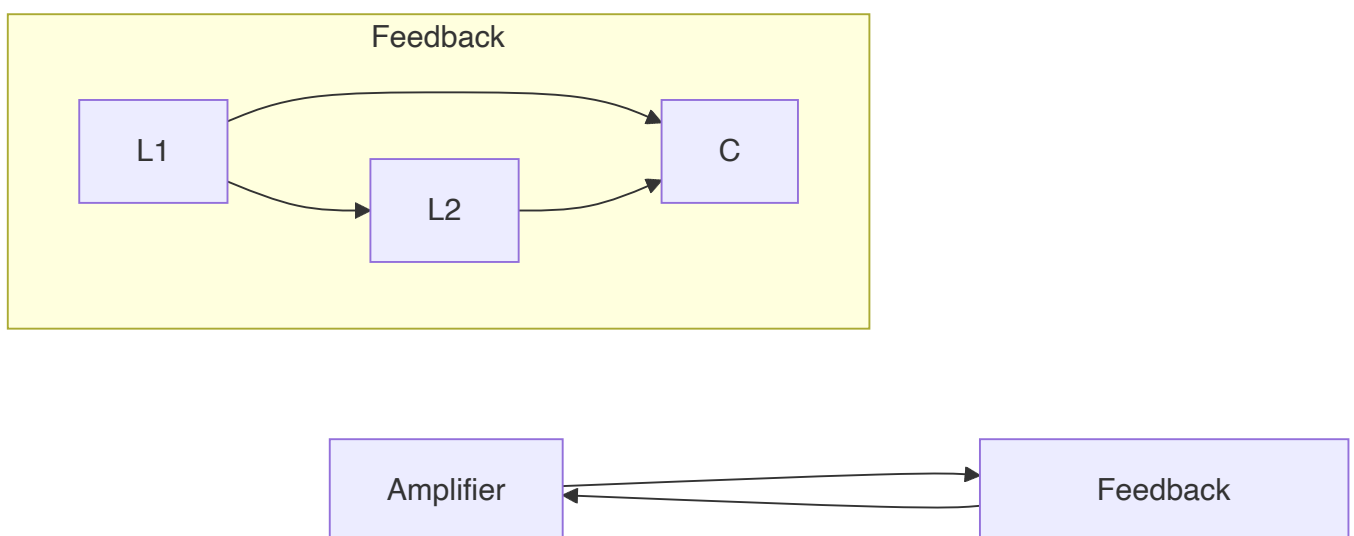Diagram:

- **Circuit components:** Amplifier, tapped inductor (L1+L2), capacitor C
- **Frequency formula:** $f = 1/[2\pi\sqrt{LC}]$ where $L = L1+L2$
- **Advantages:** Simple design, good frequency stability

- **Drawbacks:** Size of inductors, limited frequency range
- **Applications:** RF signal generators, radio receivers, communication

Mnemonic: "TILC" - "Tapped Inductor with LC Circuit"

OR


Question 2(a) [3 marks]

Explain working of transistor as a switch.

Answer:

Transistor switches between cutoff (OFF) and saturation (ON) regions for digital applications.

Diagram:

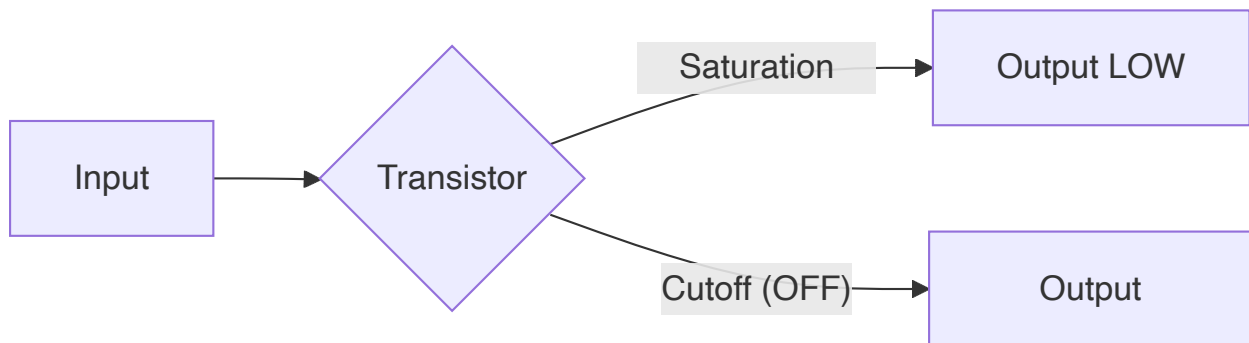

- **Cutoff region:** $V_{BE} < 0.7V$, acts as open switch, $V_{CE} \approx V_{CC}$
- **Saturation region:** $V_{BE} > 0.7V$, acts as closed switch, $V_{CE} \approx 0.2V$
- **Switching time:** Limited by junction capacitance

Mnemonic: "COPS" - "Cutoff-On-Produces Switching"


Question 2(b) [4 marks]

Define heat sink. List types of heat sink and give its applications.

Answer:

Heat sink is a thermal conductor that transfers heat away from electronic components.

Diagram:

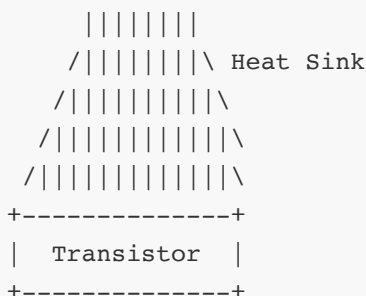

Types of Heat Sinks:

| Type | Description | Application |
|---------------|-------------------------------------|-----------------------|
| Passive | No moving parts, natural convection | Low-power devices |
| Active | With fans or pumps | High-power amplifiers |
| Liquid-cooled | Uses fluid for heat transfer | Computing systems |
| Finned | Multiple fins increase surface area | Power transistors |

- **Purpose:** Prevents thermal runaway and component failure
- **Materials:** Aluminum, copper, or alloys with high thermal conductivity

Mnemonic: "COOL" - "Conducting Out Of Local heat"

Question 2(c) [7 marks]

Explain advantages and disadvantages of negative feedback in amplifiers in detail.


Answer:

Negative feedback returns a portion of output signal to input with opposite phase.

Table:

| Advantages | Disadvantages |
|---------------------------------|--|
| Stabilizes gain | Reduces overall gain |
| Increases bandwidth | More components needed |
| Reduces distortion | More power consumption |
| Decreases noise | Complex circuit design |
| Controls input/output impedance | Potential oscillation if improperly designed |
| Improves linearity | Signal loss in feedback network |

Diagram:

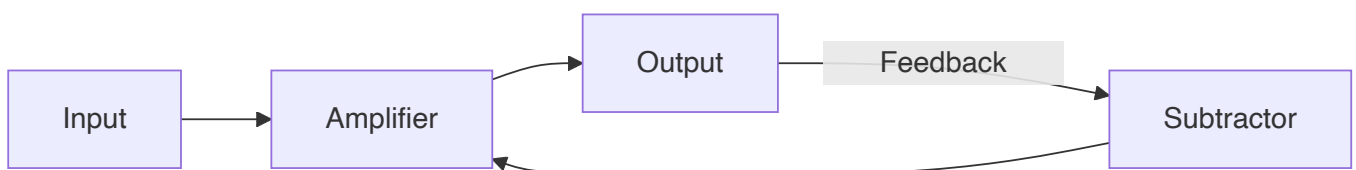

- **Gain stabilization:** Makes gain dependent on passive components
- **Bandwidth extension:** Increases by factor equal to gain reduction
- **Feedback factor:** β determines amount of improvement

Mnemonic: "STABLE" - "Stabilized Transmission And Bandwidth with Less Error"


Question 3(a) [3 marks]

Draw symbol of SCR and explain working of SCR.

Answer:

Silicon Controlled Rectifier (SCR) is a four-layer PNPN device with three terminals.

Symbol:

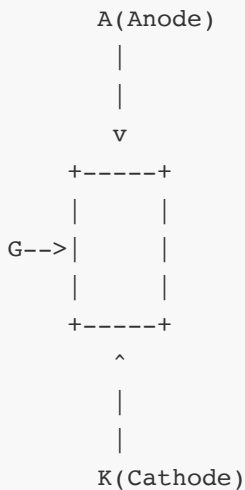

- **Structure:** P-N-P-N four-layer semiconductor device
- **Operation:** Remains OFF until gate triggered, then conducts until current falls below holding value
- **Terminals:** Anode, Cathode, Gate

Mnemonic: "AGK" - "Anode-Gate controls Kathode current"


Question 3(b) [4 marks]


Explain two transistor analogy of SCR with circuit diagram.

Answer:

SCR can be represented as interconnected PNP and NPN transistors sharing junctions.

Diagram:

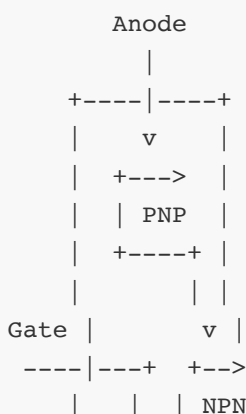

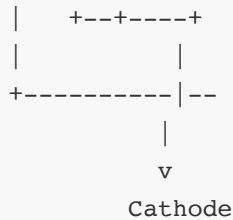

- **PNP section:** Upper transistor with collector connected to NPN base
- **NPN section:** Lower transistor with collector connected to PNP base
- **Triggering:** Small gate current turns on NPN, which turns on PNP
- **Regenerative action:** Each transistor supplies base current to other

Mnemonic: "PNPN" - "Positive-Negative-Positive-Negative layers"


Question 3(c) [7 marks]

Explain the working of TRIAC based fan regulator with circuit diagram.

Answer:

TRIAC-based fan regulator controls AC power through phase control.

Circuit Diagram:

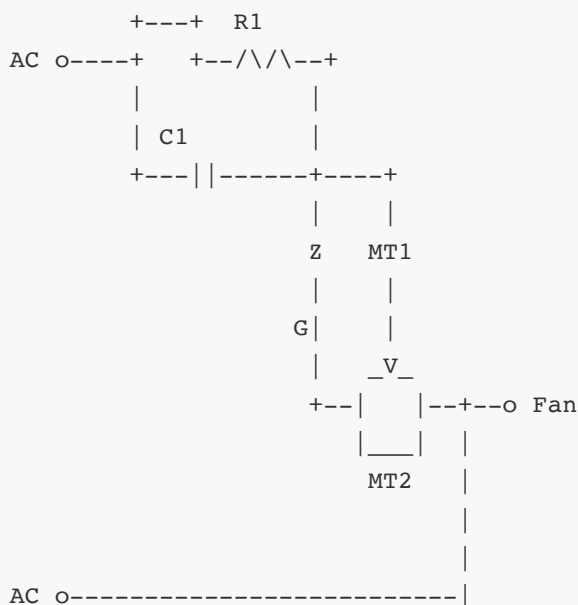


- **Phase control:** Varies firing angle of TRIAC to control power
- **Diac:** Provides bidirectional triggering for TRIAC
- **RC timing circuit:** R1 and C1 set phase delay
- **Variable resistor:** Adjusts phase delay for speed control
- **Protection:** RC snubber prevents false triggering


Mnemonic: "TRIAC" - "Triggered Response In AC Circuits"

OR**Question 3(a) [3 marks]****Draw V-I characteristics of DIAC and TRIAC.****Answer:**

DIACs and TRIACs are bidirectional devices with symmetrical characteristics.

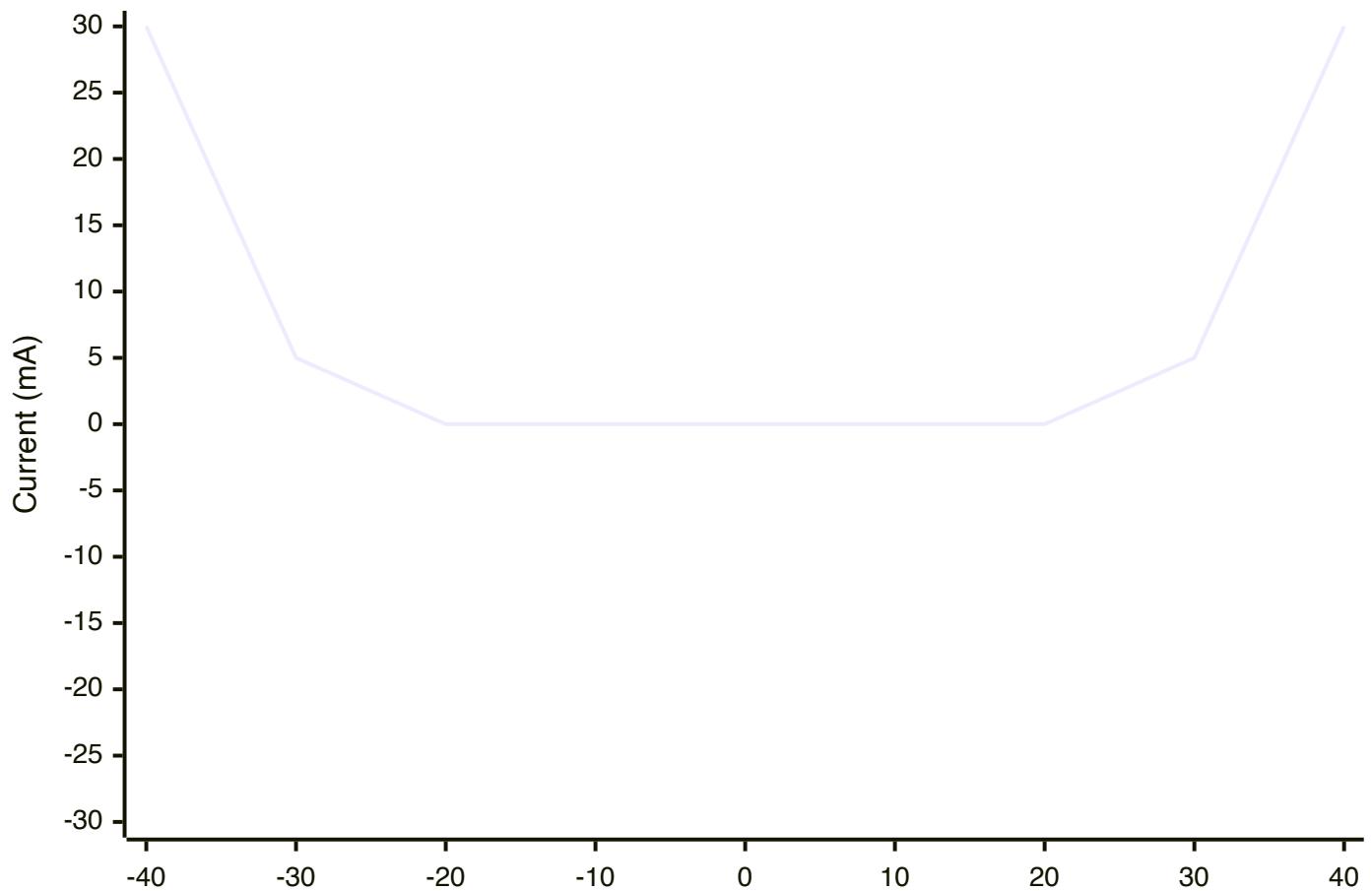DIAC Characteristics:**DIAC V-I Characteristics****TRIAC Characteristics:**

TRIAC V-I Characteristics

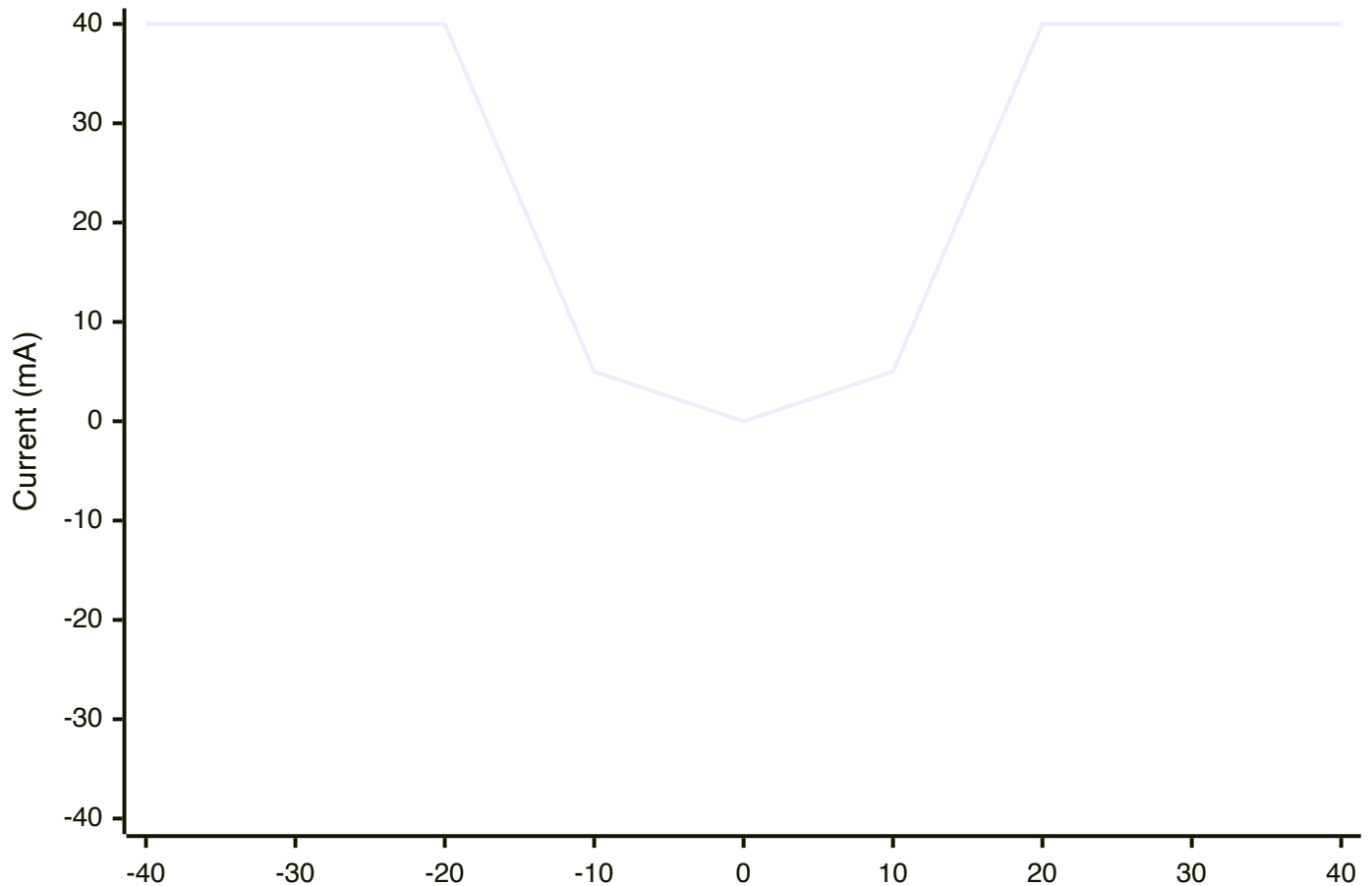

- **DIAC:** Bidirectional diode that conducts after breakover voltage
- **TRIAC:** Three-terminal device that conducts in both directions when triggered

Mnemonic: "BIBO" - "Bidirectional In, Bidirectional Out"


Question 3(b) [4 marks]

Explain the Gate triggering method of SCR.

Answer:

Gate triggering is the most common method to activate an SCR.

Diagram:

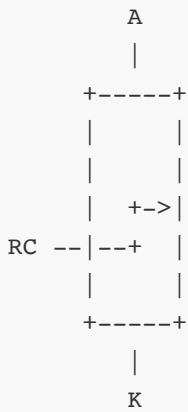

- **Gate pulse:** Small current applied between gate and cathode
- **Triggering methods:** DC, AC, or pulse signals
- **Current requirements:** Typically 5-20mA gate current
- **Advantages:** Low power control of high-power circuits

Mnemonic: "GATE" - "Gain Activation Through Electron flow"


Question 3(c) [7 marks]

Explain SCR application for DC power control.

Answer:

SCR controls DC power by chopping the supply voltage at variable duty cycles.

Circuit:

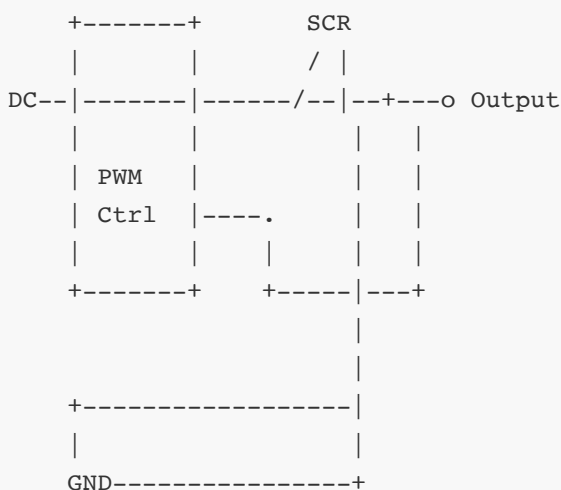

- **Phase control:** Varies firing angle to control average power
- **PWM control:** Pulse width modulation for efficient control
- **Applications:** DC motor speed control, dimming, heating
- **Advantages:** High efficiency, no moving parts, reliable
- **Limitations:** Unidirectional current flow, needs commutation

Mnemonic: "POWER" - "Pulse Operation With Electronic Regulation"

Question 4(a) [3 marks]

List characteristics of Ideal OP-AMP.

Answer:

Ideal operational amplifiers have perfect characteristics that real devices approximate.

Table:

| Characteristic | Ideal Value |
|------------------|-------------|
| Open loop gain | Infinite |
| Input impedance | Infinite |
| Output impedance | Zero |
| Bandwidth | Infinite |
| CMRR | Infinite |
| Slew rate | Infinite |
| Offset voltage | Zero |

- **Practical values:** Actual op-amps have limitations
- **Implications:** Circuit design must account for real limitations

Mnemonic: "IBOCSS" - "Infinite Bandwidth, Open-loop gain, CMRR, Slew rate, and Sensitivity"


Question 4(b) [4 marks]


Explain working of differential amplifier using OP-AMP with circuit diagram.

Answer:

Differential amplifier amplifies the voltage difference between two inputs.

Circuit:

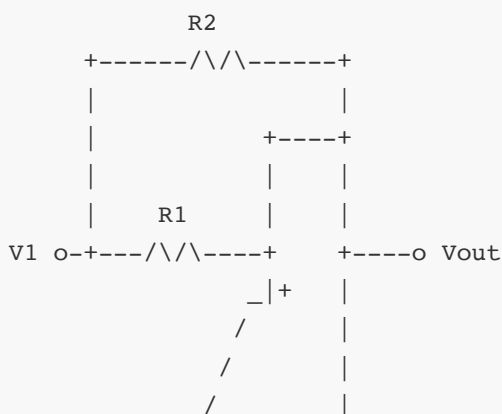

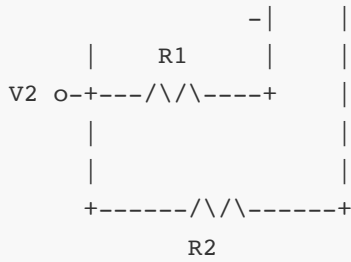

- **Gain formula:** $V_{out} = (V_1 - V_2) \times (R_2/R_1)$
- **Common mode rejection:** Suppresses signals common to both inputs
- **Applications:** Instrumentation, medical equipment, audio

Mnemonic: "DIFF" - "Dual Input For Feedback"


Question 4(c) [7 marks]

Explain OP-AMP as an inverting amplifier (Closed loop) and derive the formula of voltage gain.

Answer:

Inverting amplifier produces output that is inverted and amplified version of input.

Circuit:

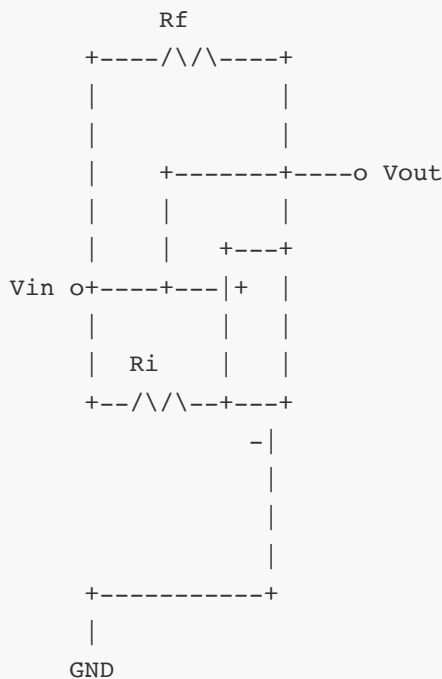

Gain Derivation:

- Apply KCL at inverting input: $I_1 + I_2 = 0$
- $I_1 = (V_{in} - V^-)/R_i$ and $I_2 = (V_{out} - V^-)/R_f$
- At virtual ground, $V^- \approx 0$
- Therefore: $V_{in}/R_i + V_{out}/R_f = 0$
- Solving for V_{out}/V_{in} : $A_v = -R_f/R_i$

- **Characteristics:** Output 180° out of phase with input
- **Feedback:** Creates virtual ground at inverting input
- **Closed loop gain:** Controlled by external resistors

Mnemonic: "VAIN" - "Virtual ground Amplification Inverts Negative"

OR

Question 4(a) [3 marks]

Define the following parameters of OPAMP:

**1) CMRR

2. Slew rate

3. Gain Bandwidth Product**

Answer:

These parameters define key performance characteristics of operational amplifiers.

Table:

| Parameter | Definition | Importance |
|------------------------|---|--------------------------------------|
| CMRR | Ratio of differential gain to common-mode gain | Higher is better for rejecting noise |
| Slew Rate | Maximum rate of output voltage change ($V/\mu s$) | Determines large-signal bandwidth |
| Gain-Bandwidth Product | Product of gain and frequency (MHz) | Measures high-frequency performance |

- **CMRR:** Typically 80-120dB in quality op-amps
- **Slew Rate:** Limits output for high-frequency, high-amplitude signals
- **GBP:** Remains constant as frequency increases

Mnemonic: "CSG" - "Common-mode rejection, Speed, and Gain"


Question 4(b) [4 marks]


Draw and explain summing amplifier using OP-AMP.

Answer:

Summing amplifier produces output proportional to weighted sum of input voltages.

Circuit:

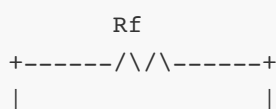

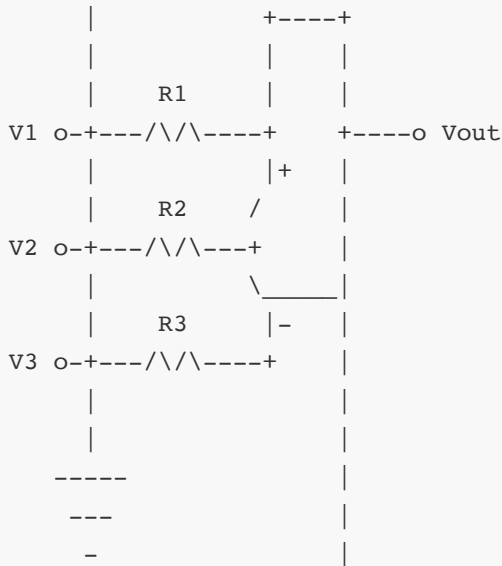

- **Output formula:** $V_{out} = -R_f(V_1/R_1 + V_2/R_2 + V_3/R_3)$
- **Applications:** Audio mixer, analog computers, signal processing
- **Advantage:** Multiple inputs can be processed simultaneously

Mnemonic: "SUM" - "Several Unified Multipliers"


Question 4(c) [7 marks]

Draw the pin diagram of IC 555 and explain Monostable multivibrator using IC555 with waveform.

Answer:


IC 555 timer in monostable mode produces a single pulse of fixed duration when triggered.

Pin Diagram:

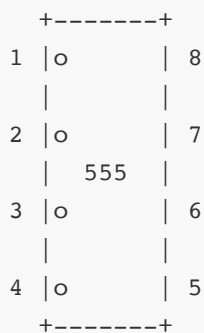

| | |
|------------|--------------|
| 1: GND | 5: Control |
| 2: Trigger | 6: Threshold |
| 3: Output | 7: Discharge |
| 4: Reset | 8: VCC |

Circuit and Waveform:

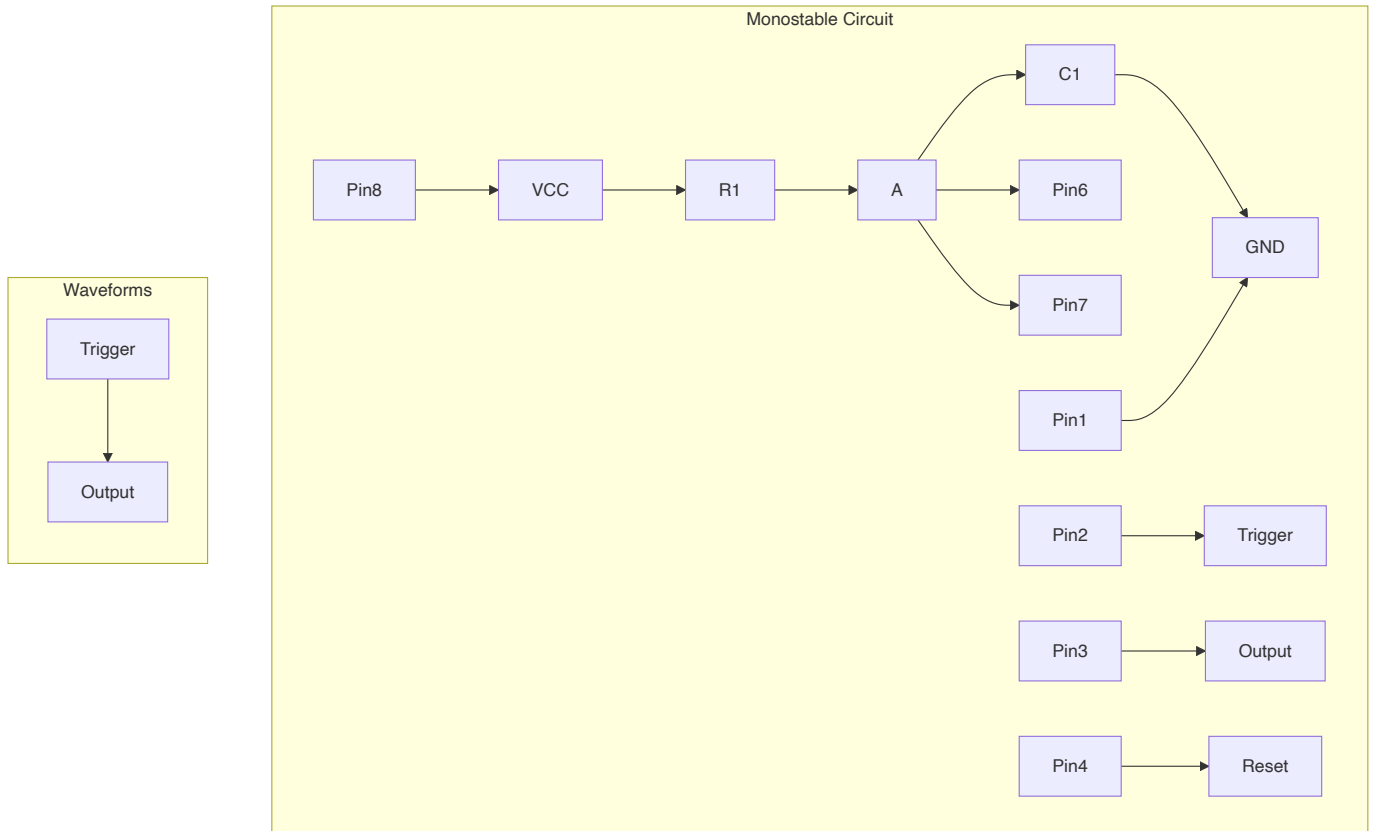

- **Operation:** Negative trigger starts timing cycle
- **Time period:** $T = 1.1 \times R \times C$
- **Applications:** Timers, pulse generation, debouncing
- **Advantages:** Simple, reliable, widely available

Mnemonic: "TIMER" - "Triggered Input Makes Extended Response"


Question 5(a) [3 marks]

Draw block diagram of SMPS and give its applications.

Answer:

Switch Mode Power Supply (SMPS) uses switching elements for efficient power conversion.

Block Diagram:

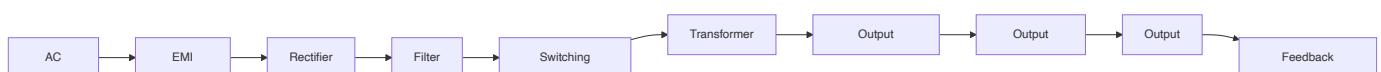

Applications:

- Computer power supplies
- Mobile phone chargers
- TV power supplies
- Industrial power systems

- LED lighting drivers
- **Advantages:** High efficiency, small size, lightweight
- **Types:** Buck, boost, buck-boost, flyback converters

Mnemonic: "SAFE" - "Switching Achieves Filtered Energy"


Question 5(b) [4 marks]

Explain working of Regulated Power Supply with diagram.

Answer:

Regulated power supply maintains constant output despite input or load variations.

Block Diagram:

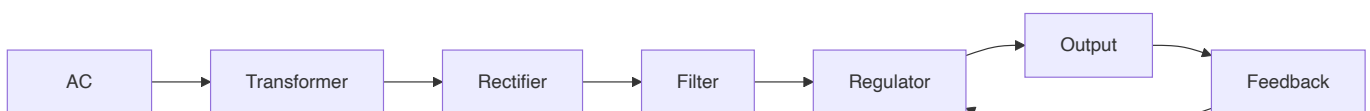

- **Transformer:** Steps down AC voltage to required level
- **Rectifier:** Converts AC to pulsating DC (diode bridge)
- **Filter:** Smooths DC with capacitors
- **Regulator:** Maintains constant output voltage
- **Feedback:** Compensates for input/load variations

Mnemonic: "TRFRO" - "Transform, Rectify, Filter, Regulate, Output"


Question 5(c) [7 marks]

Explain basic block diagram of OP-AMP with diagram.

Answer:

Operational amplifier's internal structure consists of several stages performing specific functions.

Block Diagram:

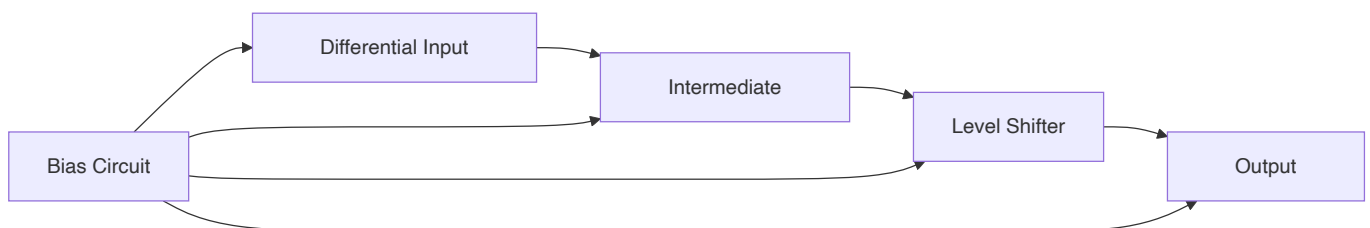

- **Differential input stage:** High impedance, amplifies difference
- **Intermediate stage:** Provides additional gain
- **Level shifter:** Adjusts DC level between stages
- **Output stage:** Low impedance, current amplification

- **Bias circuit:** Establishes operating points for all stages
- **Compensation:** Internal capacitor for stability

Mnemonic: "DILO" - "Differential Input, Level shift, Output"

OR


Question 5(a) [3 marks]

Explain adjustable voltage regulator using LM317 with diagram.

Answer:

LM317 is a versatile adjustable positive voltage regulator with output range of 1.25V to 37V.

Circuit:

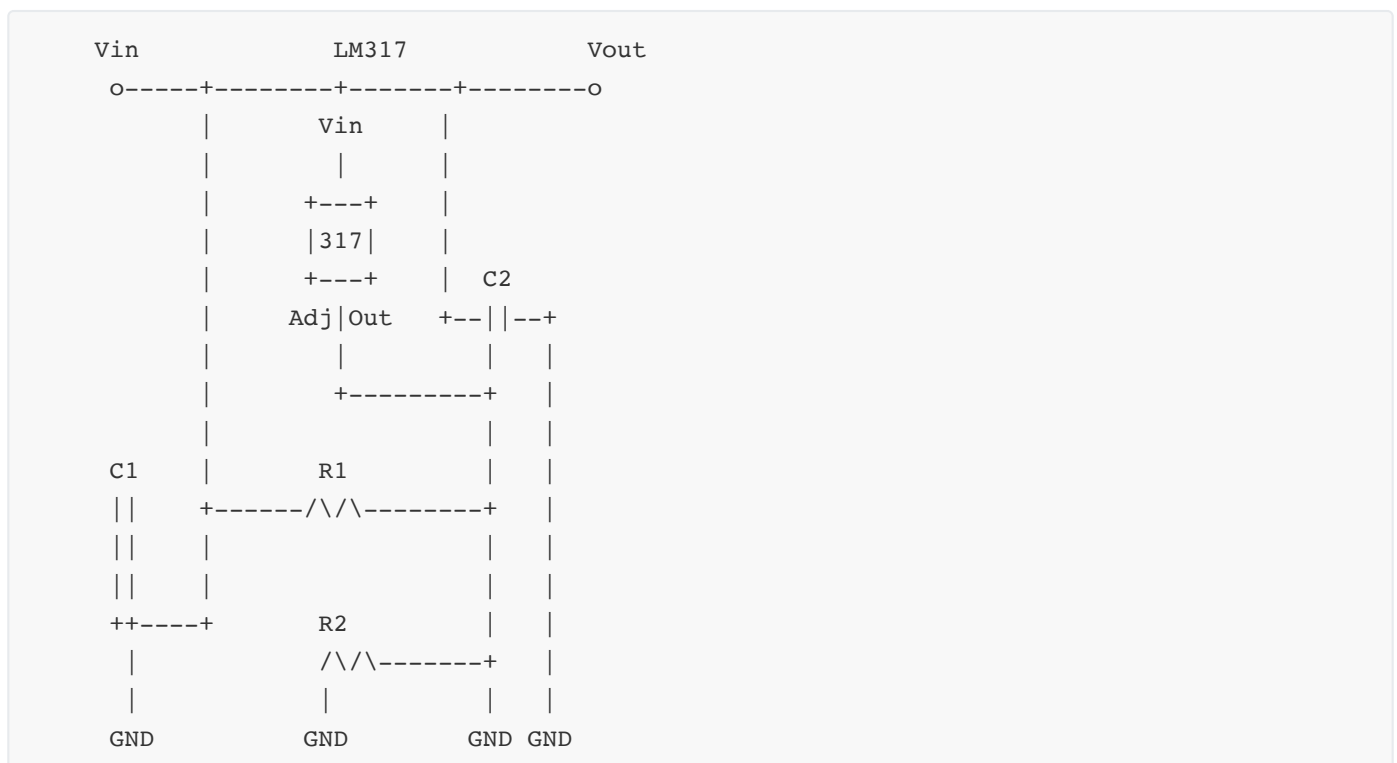

- **Formula:** $V_{out} = 1.25(1 + R2/R1)$
- **Advantages:** Simple adjustment, built-in protection
- **Applications:** Variable power supplies, battery chargers

Mnemonic: "AVR" - "Adjustable Voltage Regulation"

Question 5(b) [4 marks]

Give the difference between Fixed voltage regulator IC and Variable voltage regulator IC.

Answer:

Voltage regulator ICs differ in their configurability and application requirements.

Table:

| Parameter | Fixed Voltage Regulator | Variable Voltage Regulator |
|---------------------|----------------------------------|-------------------------------------|
| Output voltage | Predetermined (e.g., 5V, 12V) | Adjustable over a range |
| External components | Minimal (capacitors only) | Requires resistors for setting |
| Series | 78xx (positive), 79xx (negative) | LM317 (positive), LM337 (negative) |
| Applications | Standard equipment | Custom designs, laboratory supplies |
| Flexibility | Limited to fixed values | Highly adaptable |
| Pin count | Typically 3 pins | 3 or more pins |

- **Fixed regulators:** Simple to use, limited adjustment
- **Variable regulators:** More versatile, require calculation

Mnemonic: "FOCUS" - "Fixed Output Compared to User-Set"

Question 5(c) [7 marks]

List applications of OP-AMP. Explain working operation of D to A converter with circuit diagram using OP-AMP.


Answer:


Op-amps have numerous applications; D/A converters transform digital signals to analog.

Applications of OP-AMP:

- Amplifiers (inverting, non-inverting)
- Filters (active filters)
- Oscillators
- Comparators
- Integrators and differentiators
- Voltage followers
- Instrumentation circuits

R-2R Ladder DAC Circuit:

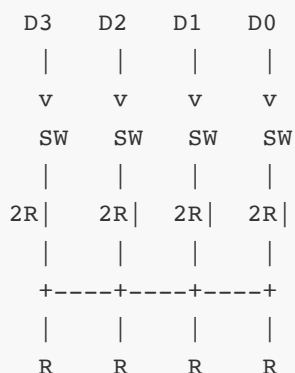

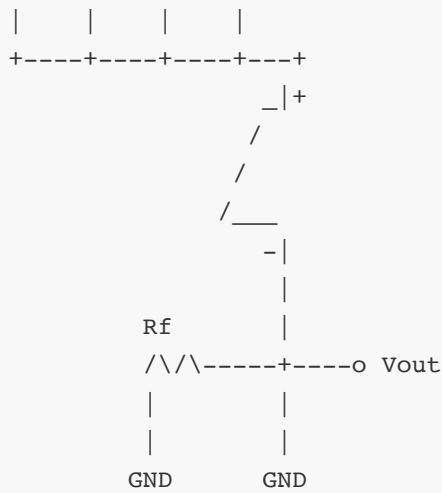

- **Working principle:** Digital inputs weight currents through resistor network
- **Resistance values:** Binary-weighted or R-2R ladder network
- **Conversion:** Output voltage proportional to digital input value
- **Resolution:** Determined by number of bits (2^n levels)

Mnemonic: "DART" - "Digital to Analog Resistor Translation"